

# 9702 C19 Capacitance



# Capacitors and capacitance

Capacitors are electrical devices used to store energy in circuits (commonly for a backup release of energy if the power fails)

Capacitors can be in the form of:

1. An isolated spherical conductor
2. Parallel plates

Capacitance = quantity of the **charge stored per unit potential difference**


$$C = \frac{Q}{V}$$

C=capacitance (F=farad)

Q=charge (C)

V=potential difference(V)

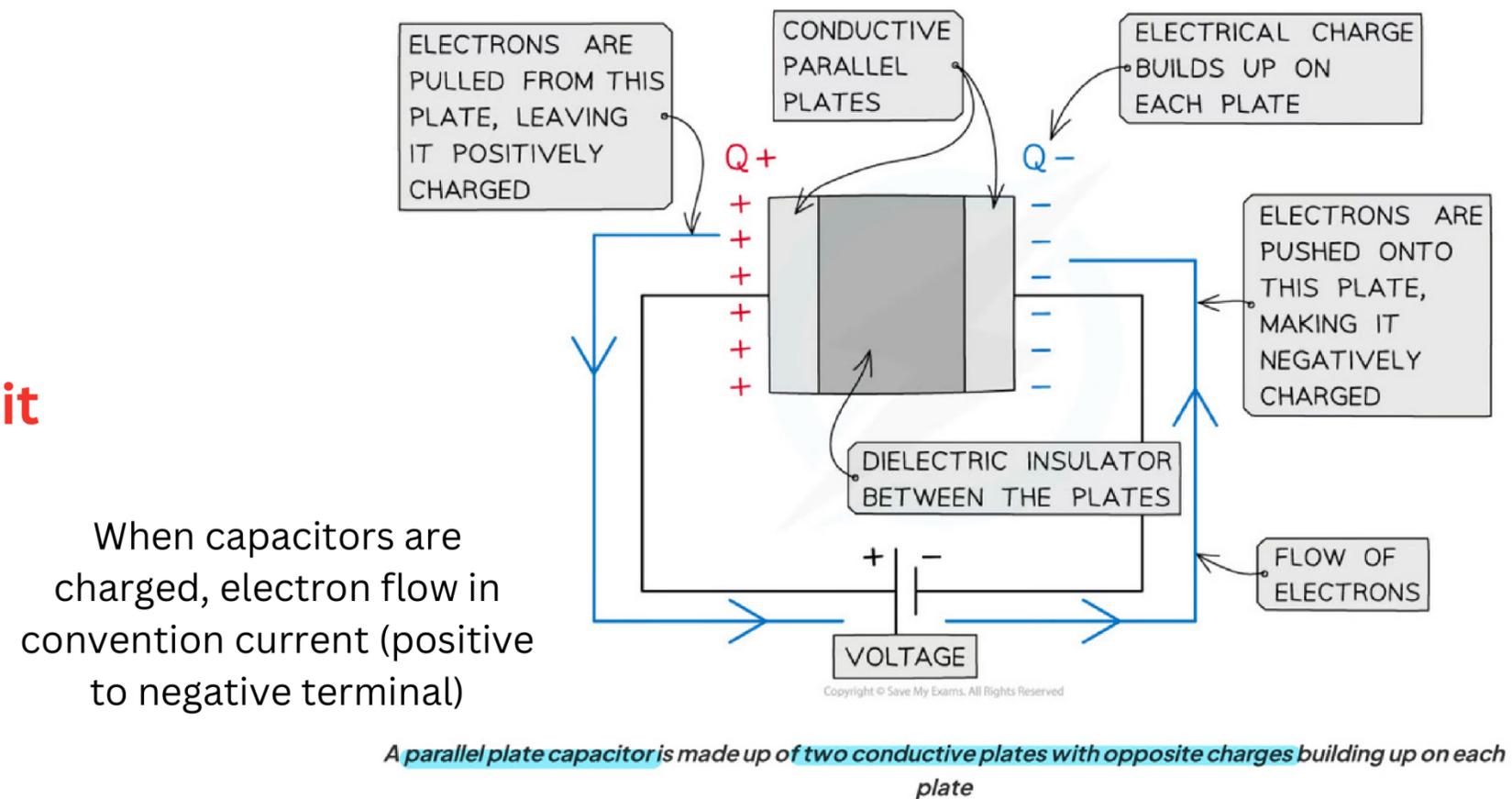(C is often written in microfarad and nanofarad)



Q is NOT the charge of the capacitor itself, it is the charge stored ON the plates or spherical conductors

# Capacitance of a Spherical Conductor

- The potential  $V$  is defined by the potential of an isolated point charge (since the charge on the surface of a spherical conductor can be considered as a point charge at its centre):

$$V = \frac{Q}{4\pi\epsilon_0 r} = \frac{kQ}{r}$$

$$\left( k = \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 \text{ mF}^{-1} \right)$$

- Substituting this into the capacitance equation means the capacitance  $C$  of a sphere is given by the expression:

$$C = 4\pi\epsilon_0 r = \frac{r}{k}$$

# Derivation of $C=Q/V$ in series and parallel

The circuit symbol for a parallel plate capacitor is two parallel lines




<u>series</u>	<u>parallel</u>
① $V = V_1 + V_2 + \dots$	① $Q = Q_1 + Q_2 + \dots$
② $V_1 = \frac{Q}{C_1} \quad V_2 = \frac{Q}{C_2}$	② $Q_1 = C_1 V \quad Q_2 = C_2 V$
③ $V = \frac{Q}{C_{total}}$	③ $Q = C_{total} V$
$\frac{Q}{C_{total}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \dots$	$C_{total} V = C_1 V + C_2 V + \dots$ $= (C_1 + C_2 + \dots) V$
④ $\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$	④ $C_{total} = C_1 + C_2 + \dots$

# Area under a Potential-Charge Graph


When charging a capacitor, the power supply pushes electrons from + to - plate --> work is done on the electrons, which increase electric potential energy

Adding more e<sup>-</sup> to the negative plate at first is easy because there is little repulsion, but as the e<sup>-</sup> builds up, more work is required to overcome higher repulsion

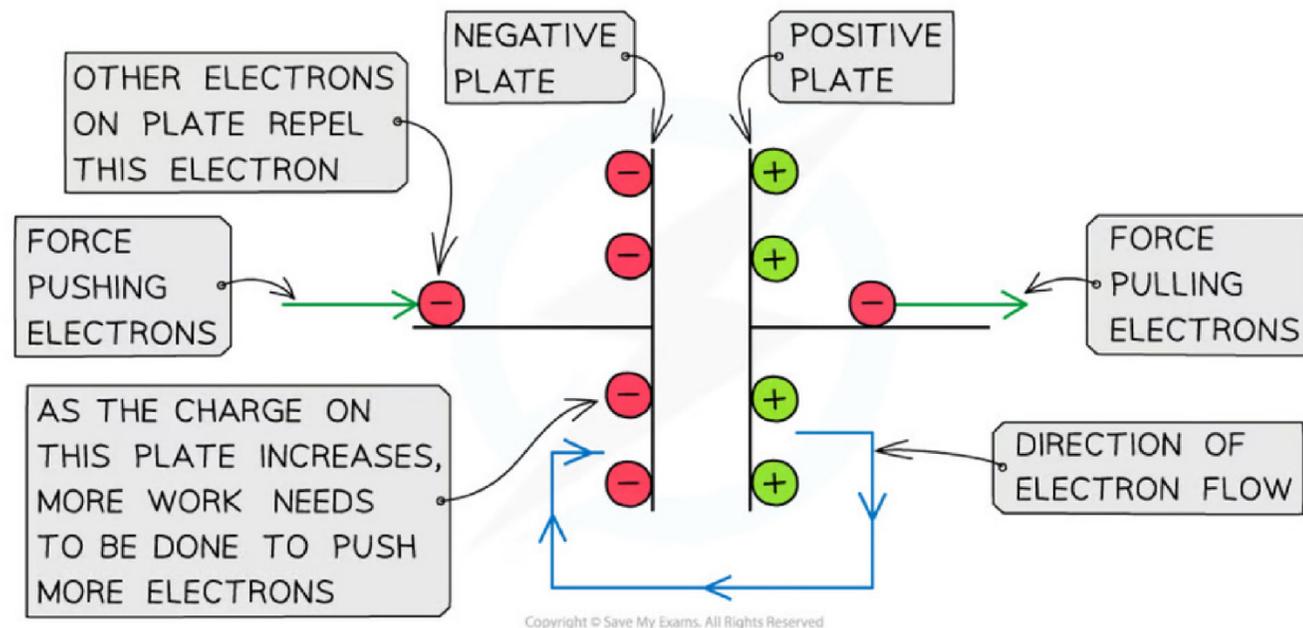-->The greater amount of work must be done to increase the charge on the negative plate (i.e. **the potential difference V across the capacitor increases as the amount of charge Q increases**)


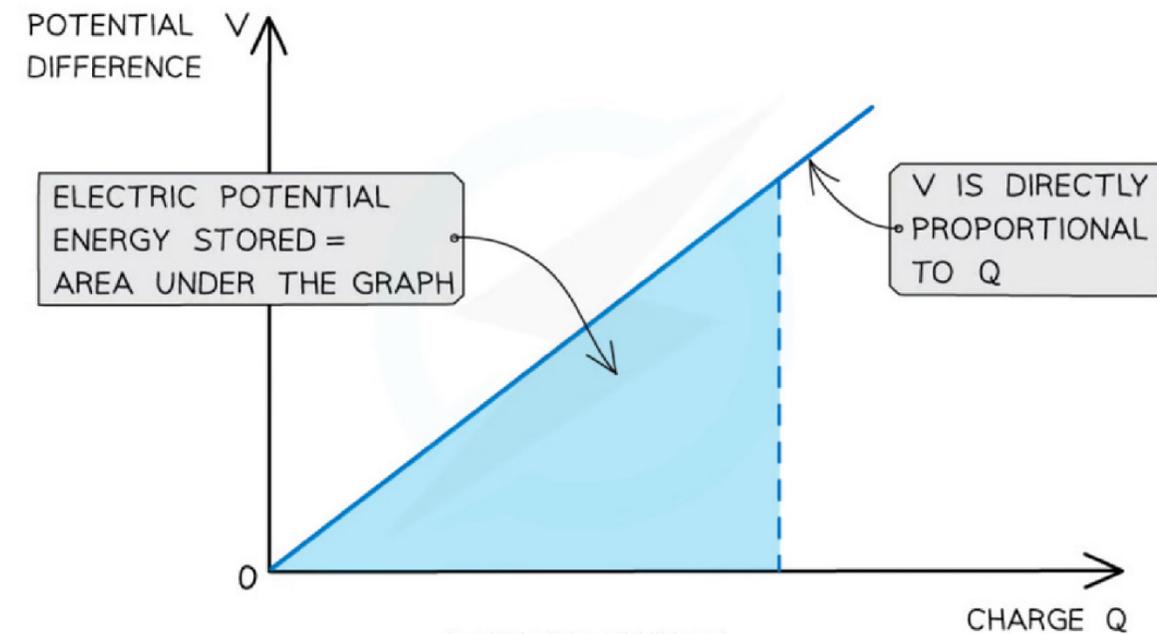
$$\text{electric potential energy} = \text{Area} = \frac{1}{2} \times \text{base} \times \text{height} = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$



# Capacitor Discharging Graph



Capacitors are discharged through a resistor

-->the electrons now flow back from negative to positive plate until it reaches equilibrium (when there are equal number of  $e^-$  on each plate)

**at the start of discharge, the current is large and current, p.d. and charge all decrease exponentially to zero**

(this means rate at which the current, p.d. or charge decreases is proportional to the amount of current, p.d. or charge it has left)

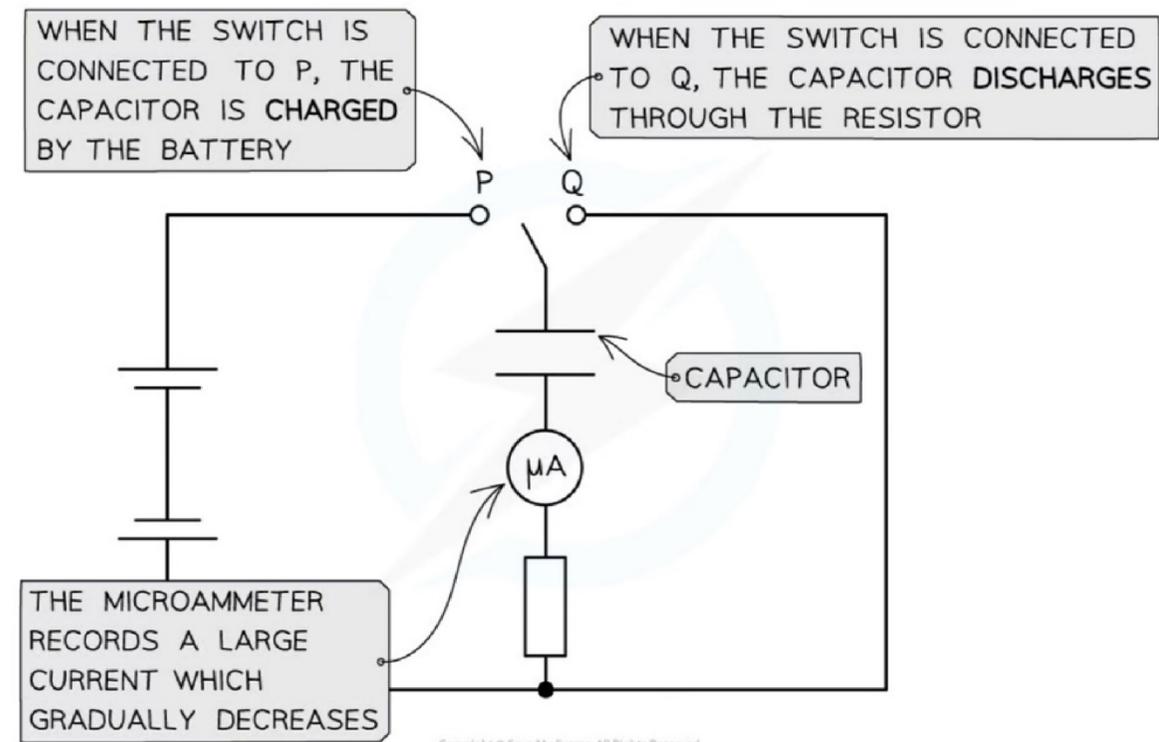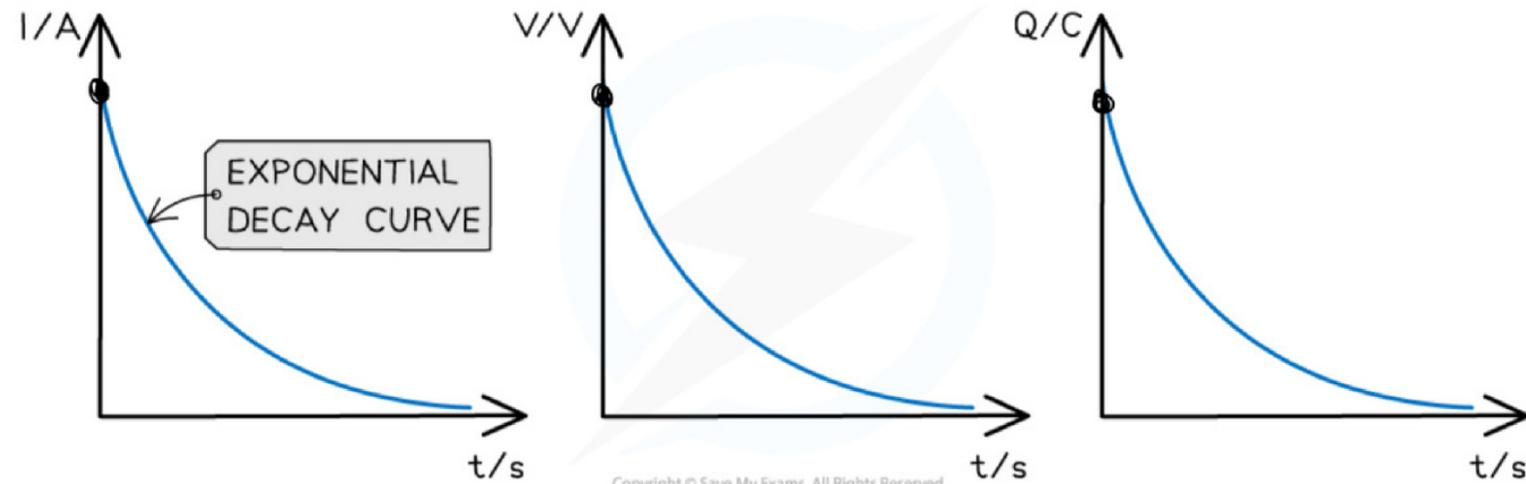**high resistance = current decrease = charge flow slowly = capacitor take longer to discharge**



# Capacitor Discharge Equations


Time constant of a capacitor discharging is represented by 'tau' ( $\tau$ )

**time constant = time taken for the charge of a capacitor to decrease to 0.37(1/e) of its original value**

$$\tau = RC$$

Where:

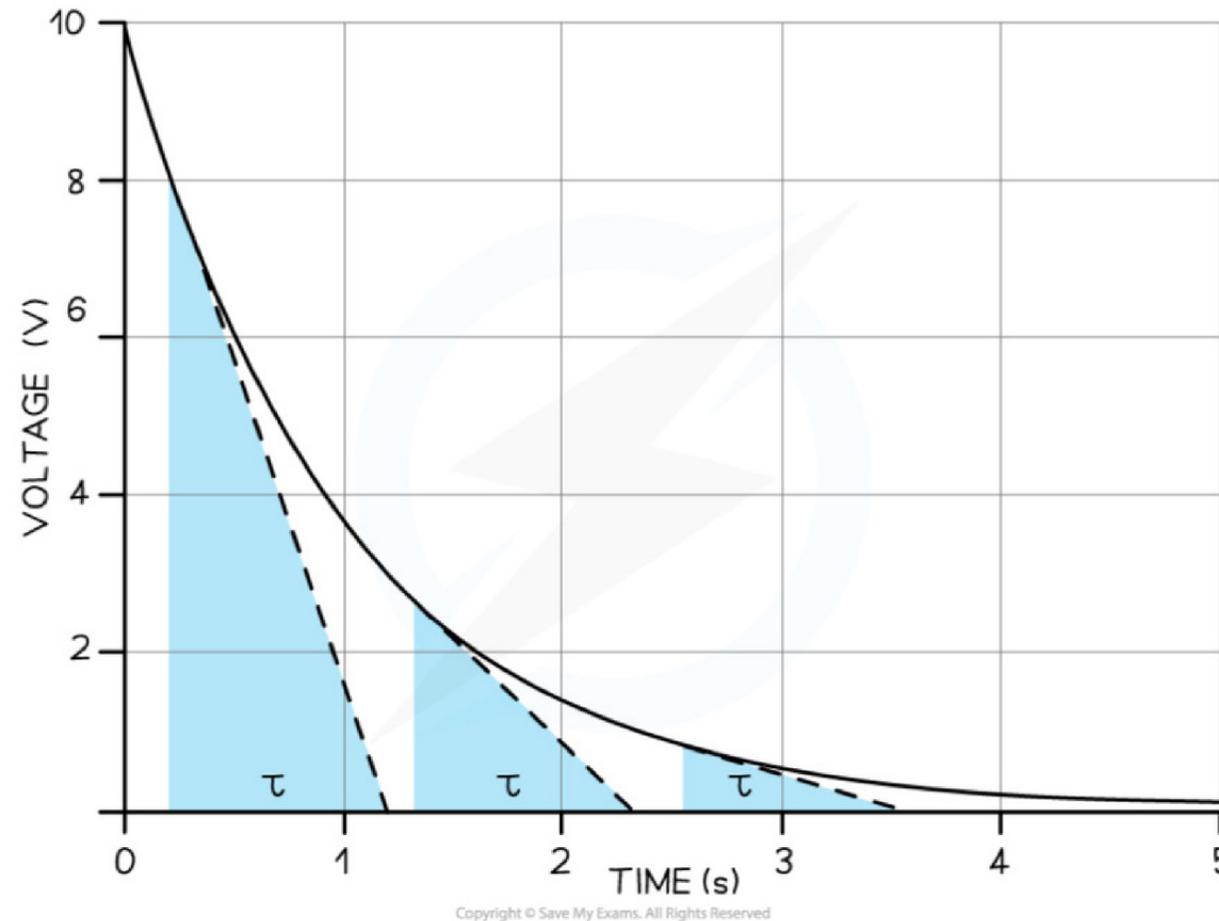- $\tau$  = time constant (s)
- R = resistance of the resistor ( $\Omega$ )
- C = capacitance of the capacitor (F)



*The graph of voltage-time for a discharging capacitor showing the positions of the first three time constants*

$$I = I_0 e^{-\frac{t}{RC}}$$

$$V = V_0 e^{-\frac{t}{RC}}$$

$$Q = Q_0 e^{-\frac{t}{RC}}$$

Where:

- $I$  = current (A)
- $I_0$  = initial current before discharge (A)
- $e$  = the exponential function
- $t$  = time (s)
- $RC$  = resistance ( $\Omega$ )  $\times$  capacitance (F) = the time constant  $\tau$  (s)