

- 5 A solid metal sphere, of radius  $r$ , is insulated from its surroundings. The sphere has charge  $+Q$ . This charge is on the surface of the sphere but it may be considered to be a point charge at its centre, as illustrated in Fig. 5.1.

For  
Examiner's  
Use

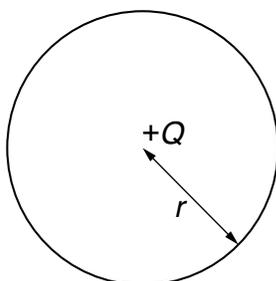


Fig. 5.1

$$C = Q/V$$

- (a) (i) Define *capacitance*.

Charge stored per unit potential  
difference.

[1]

- (ii) Show that the capacitance  $C$  of the sphere is given by the expression

$$C = 4\pi\epsilon_0 r.$$

$$C = \frac{q}{V} \quad \text{as } V = \frac{q}{4\pi\epsilon_0 r}$$

$$C = q \div \frac{q}{4\pi\epsilon_0 r}$$

$$C = \cancel{q} \times \frac{4\pi\epsilon_0 r}{\cancel{q}}$$

$$C = 4\pi\epsilon_0 r$$

[1]

- (b) The sphere has radius 36 cm. Determine, for this sphere,

- (i) the capacitance,

$$C = 4\pi\epsilon_0 r$$

$$C = 4\pi (8.85 \times 10^{-12}) (36 \times 10^{-2})$$

capacitance =  $4.0 \times 10^{-11}$  F [1]

- (ii) the charge required to raise the potential of the sphere from zero to  $7.0 \times 10^5$  V.

$$q = CV$$

$$\Delta q = C\Delta V$$

$$\Delta q = (4 \times 10^{-11}) (7 \times 10^5)$$

$$\text{charge} = \dots\dots\dots 2.8 \times 10^{-5} \dots\dots\dots \text{ C [1]}$$

- (c) Suggest why your calculations in (b) for the metal sphere would not apply to a plastic sphere.

*Most Spheres are conductors and charge in them is uniformly distributed so they can be treated as point charges. Plastic is an insulator. Its charges is either at surface or at centre.*

[3]

- (d) A spark suddenly connects the metal sphere in (b) to the Earth, causing the potential of the sphere to be reduced from  $7.0 \times 10^5$  V to  $2.5 \times 10^5$  V.

Calculate the energy dissipated in the spark.

$$E = \frac{1}{2}CV^2$$

$$\Delta E = \frac{1}{2}C \left( V_F^2 - V_i^2 \right)$$

$$\text{energy} = \dots\dots\dots 8.6 \dots\dots\dots \text{ J [3]}$$

$$\frac{1}{2} \times 4 \times 10^{-11} \times \left[ (2.5 \times 10^5)^2 - (7 \times 10^5)^2 \right]$$

5 (a) State two functions of capacitors in electrical circuits.

1. .... STORE ENERGY .....
2. .... USED IN TUNING CIRCUITS .....

[2]

(b) Three capacitors, each marked '30 μF, 6V max', are arranged as shown in Fig. 5.1.


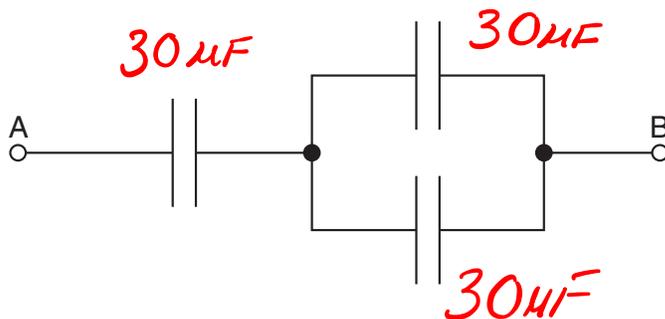


Fig. 5.1

Determine, for the arrangement shown in Fig. 5.1,

(i) the total capacitance,

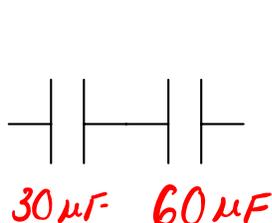

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_T} = \frac{1}{30} + \frac{1}{60}$$


20

capacitance = ..... μF [2]

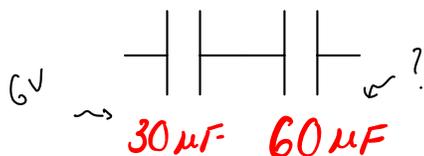(ii) the maximum potential difference that can safely be applied between points A and B.

$q = CV$   
 $q$  same in series

$q_1 = q_2$   
 $C_1 V_1 = C_2 V_2$   
 $30 \times 6 = 60 \times V_2$   
 $V_2 = 3V$   
 $max V = 6 + 3 = 9V$



$\downarrow C \propto \frac{1}{V} \uparrow$  Smaller "C" more "V"

We assume max 6V on smallest capacitor i.e 30 μF

potential difference = ..... V [2]

Ratio :-  $C_1 V_1 = C_{TOTAL} V_{AB}$   
 $(30 \times 10^{-6})(6) = (20 \times 10^{-6}) V_{AB}$

$V_{AB} = 9V$

- (c) A capacitor of capacitance  $4700\ \mu\text{F}$  is charged to a potential difference of  $18\text{V}$ . It is then partially discharged through a resistor. The potential difference is reduced to  $12\text{V}$ . Calculate the energy dissipated in the resistor during the discharge.



For  
Examiner's  
Use

$$\Delta E = \frac{1}{2} C (V_f^2 - V_i^2)$$

$$\frac{1}{2} (4700 \times 10^{-6}) (12^2 - 18^2)$$


-0.423

energy = ..... 0.42 J [3]

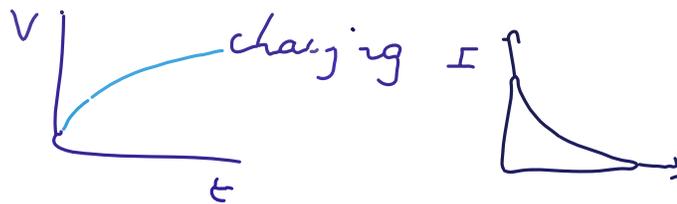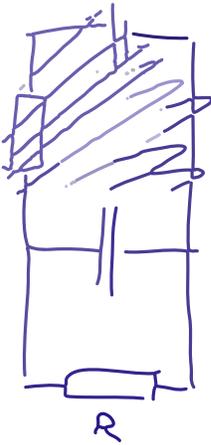

DISCHARGING

$$\frac{V}{V_0} = e^{-\frac{t}{RC}}$$

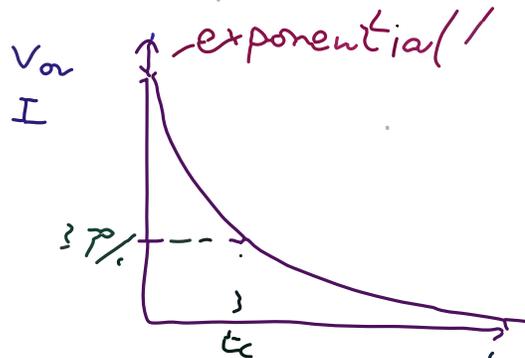

When  $t = RC$ ,  $e^{-1} = 0.37$  (37%)

$RC = \text{time constant! } (t_c)$

$$\ln\left(\frac{V}{V_0}\right) = -\frac{t}{RC}$$

- 7 A student sets up the circuit shown in Fig. 7.1 to measure the charge on a capacitor  $C$  for different values of potential difference across the capacitor.

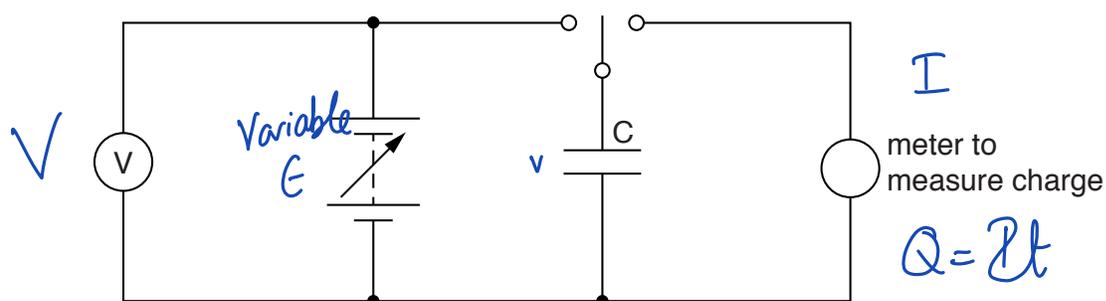


Fig. 7.1

The variation with potential difference  $V$  of the charge  $Q$  stored on the capacitor is shown in Fig. 7.2.

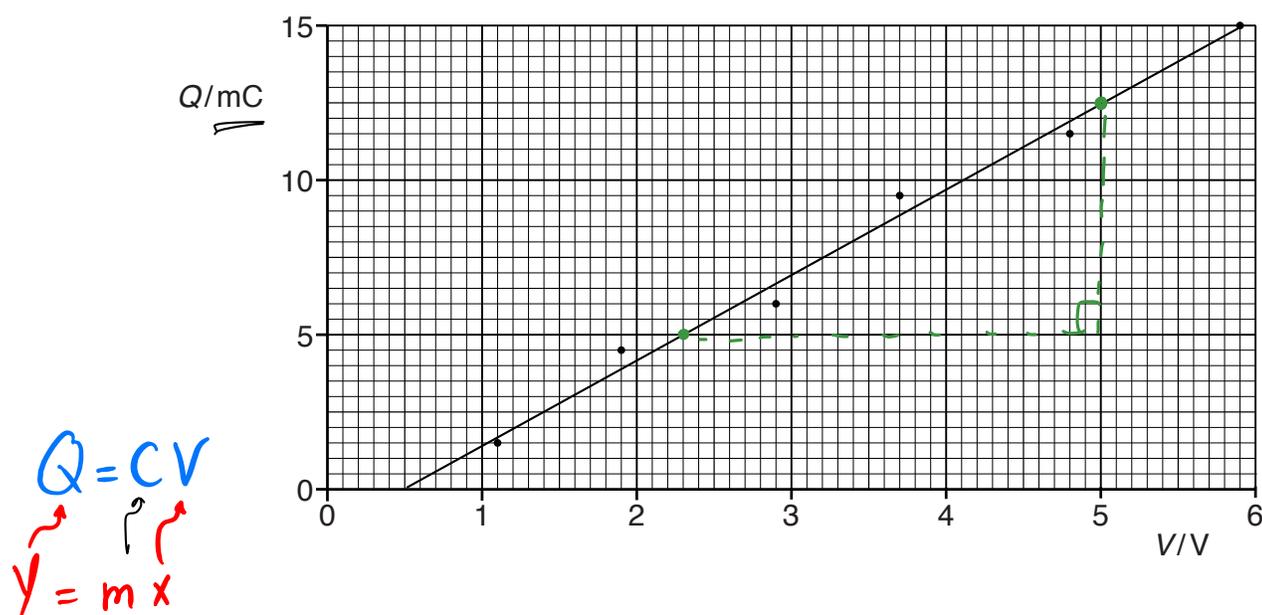


Fig. 7.2

- (a) State and explain how Fig. 7.2 indicates that there is a systematic error in the readings of one of the meters.

Based on  $Q = CV$ ,  $Q \propto V$ . But the graph does not pass through origin

[2]

- (b) Use Fig. 7.2 to determine the capacitance, in  $\mu\text{F}$ , of capacitor C.

$$C = \text{gradient}$$

$$C = \frac{y_2 - y_1}{x_2 - x_1}$$

$$C = \frac{(12.5 - 5) \times 10^{-3}}{5 - 2.3} = 2780 \times 10^{-6}$$

capacitance = ..... **2800** .....  $\mu\text{F}$  [3]

- (c) Use your answer in (b) to determine the additional energy stored in the capacitor C when the potential difference across it is increased from 6.0V to 9.0V.

$$\Delta E = \frac{1}{2} C \{V_f^2 - V_i^2\}$$

$$\Delta E = \frac{1}{2} (2780 \times 10^{-6}) (6^2 - 9^2) = -0.06255$$

$$6.255 \times 10^{-2}$$

energy = .....  **$6.3 \times 10^{-2}$**  ..... J [3]

[Total: 8]

$$Q = CV \quad C = Q/V$$

10

- 4 (a) Define capacitance.

Ratio of charge stored to potential difference across it.

For  
Examiner's  
Use

[1]

- (b) An isolated metal sphere has a radius  $r$ . When charged to a potential  $V$ , the charge on the sphere is  $q$ .  
The charge may be considered to act as a point charge at the centre of the sphere.

- (i) State an expression, in terms of  $r$  and  $q$ , for the potential  $V$  of the sphere.

$$V = \frac{1}{4\pi\epsilon_0} \frac{q}{r}$$

[1]

- (ii) This isolated sphere has capacitance. Use your answers in (a) and (b)(i) to show that the capacitance of the sphere is proportional to its radius.

$$q = CV$$

$$C = \frac{q}{V} = \frac{q}{\left(\frac{q}{4\pi\epsilon_0 r}\right)}$$

$$C = 4\pi\epsilon_0 r$$

$4\pi\epsilon_0$  is constant so,

$$C \propto r$$

[1]

- (c) The sphere in (b) has a capacitance of 6.8 pF and is charged to a potential of 220V.

Calculate

- (i) the radius of the sphere,

$$C = 4\pi\epsilon_0 r$$

$$\frac{C}{4\pi\epsilon_0} = r$$

$$\frac{6.8 \times 10^{-12}}{4\pi(8.85 \times 10^{-12})}$$

radius =  $6.1 \times 10^{-2}$  m [3]

- (ii) the charge, in coulomb, on the sphere.

$$Q = CV = 6.8 \times 10^{-12} \times 220$$

$$\text{charge} = \dots\dots\dots 1.50 \times 10^{-9} \text{ C [1]}$$

- (d) A second uncharged metal sphere is brought up to the sphere in (c) so that they touch. The combined capacitance of the two spheres is 18 pF.

Calculate

- (i) the potential of the two spheres,

$$\left. \begin{array}{l} Q = CV \\ \frac{Q}{c} = V \end{array} \right\} \frac{1.5 \times 10^{-9}}{18 \times 10^{-12}} = V$$

$$\text{potential} = \dots\dots\dots 83 \text{ V [1]}$$

- (ii) the change in the total energy stored on the spheres when they touch.

$$\Delta E = \frac{1}{2} Q (v_f - v_i)$$

$$\frac{1}{2} \times (1.5 \times 10^{-9}) (83 - 220)$$

$$\text{change} = \dots\dots\dots 1.03 \times 10^{-7} \text{ J [3]}$$

$$Q = CV$$

$$C = Q/V$$

12

- 7 (a) Explain what is meant by the *capacitance* of a parallel plate capacitor.

Ratio of charge stored on one plate of capacitor to the p.d across plates.

[3]

- (b) A parallel plate capacitor C is connected into the circuit shown in Fig. 7.1.

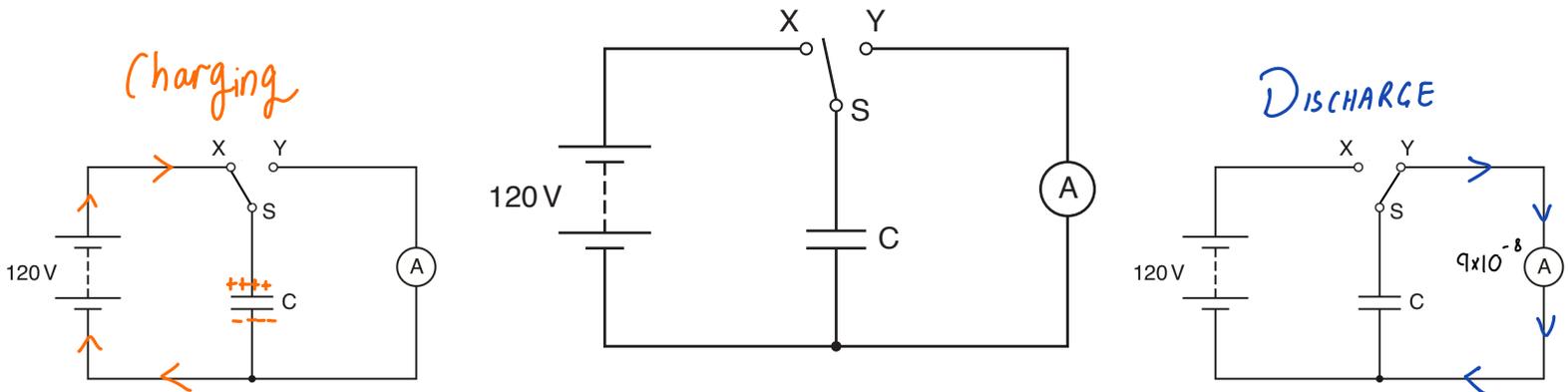


Fig. 7.1

When switch S is at position X, the battery of electromotive force 120 V and negligible internal resistance is connected to capacitor C.

When switch S is at position Y, the capacitor C is discharged through the sensitive ammeter.

The switch vibrates so that it is first in position X, then moves to position Y and then back to position X fifty times each second.

The current recorded on the ammeter is  $4.5 \mu\text{A}$ .

$$\frac{1}{50} = 0.02 \text{ s}$$

Determine

- (i) the charge, in coulomb, passing through the ammeter in 1.0 s,

$$Q = It = 4.5 \times 10^{-6} \times 1$$

charge =  $4.5 \times 10^{-6}$  C [1]

- (ii) the
- charge on one plate of the capacitor, each time that it is charged,

$$Q_{\text{TOTAL}} = 4.5 \times 10^{-6}$$

$$Q = \frac{4.5 \times 10^{-6}}{50}$$

$$\text{charge} = \dots\dots\dots 9.0 \times 10^{-8} \dots\dots\dots \text{C [1]}$$

- (iii) the capacitance of capacitor C.

$$C = \frac{Q}{V} \qquad C = \frac{9 \times 10^{-8}}{120}$$

$$\text{capacitance} = \dots\dots\dots 7.5 \times 10^{-10} \dots\dots\dots \text{F [2]}$$


- (c) A second capacitor, having a capacitance equal to that of capacitor C, is now placed in series with C.

Suggest and explain the effect on the current recorded on the ammeter.

Total Capacitance is halved (less total charge passing ammeter) so current halved.

..... [2]

[Total: 9]

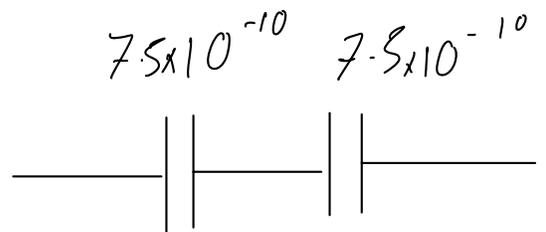

$$C_{\text{TOT}} = 3.75 \times 10^{-10}$$

$$\downarrow C = \frac{Q}{V} \downarrow$$

(A)  $\rightarrow \frac{1}{2}$  current!

- 6 (a) Explain what is meant by the *capacitance* of a parallel plate capacitor.


Capacitance is ratio of charge on a single plate of a capacitor to the potential difference b/w the plates of the capacitor.

[3]

- (b) Three parallel plate capacitors each have a capacitance of 6.0 μF.

Draw circuit diagrams, one in each case, to show how the capacitors may be connected together to give a combined capacitance of


- (i) 9.0 μF,

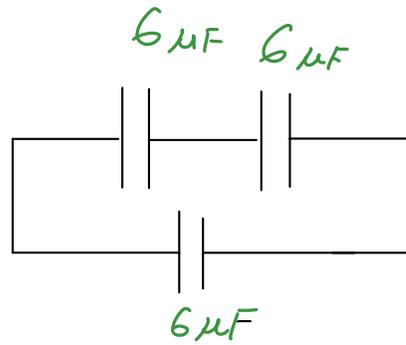

$$\left(\frac{1}{6} + \frac{1}{6}\right)^{-1} + 6 = 9 \mu F$$

[1]

- (ii) 4.0 μF.

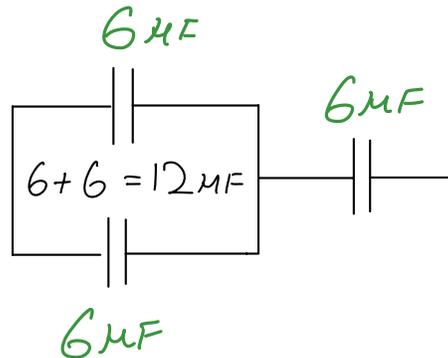

$$\left(\frac{1}{12} + \frac{1}{6}\right)^{-1} = 4 \mu F$$

[1]

- (c) Two capacitors of capacitances 3.0 μF and 2.0 μF are connected in series with a battery of electromotive force (e.m.f.) 8.0 V, as shown in Fig. 6.1.

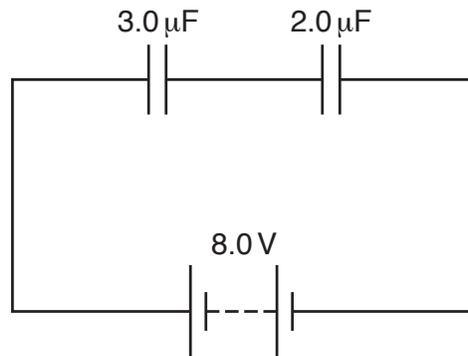


Fig. 6.1

- (i) Calculate the combined capacitance of the capacitors.

$$C_T = \left( \frac{1}{3} + \frac{1}{2} \right)^{-1}$$

capacitance = ..... **1.2** .....  $\mu\text{F}$  [1]

- (ii) Use your answer in (i) to determine, for the capacitor of capacitance  $3.0 \mu\text{F}$ ,

1. the charge on one plate of the capacitor,

$$C = \frac{Q}{V}; Q = CV$$

$$Q = (1.2 \times 10^{-6}) (8)$$

charge = ..... **9.6** .....  $\mu\text{C}$

2. the energy stored in the capacitor.

$$E = \frac{1}{2} QV$$

$$\therefore V = \frac{Q}{C} = \frac{9.6 \times 10^{-6}}{3.0 \times 10^{-6}} = 3.2 \text{ V}$$

$$\frac{1}{2} (9.6 \times 10^{-6}) (3.2)$$

OR

energy = .....  **$1.5 \times 10^{-5}$**  ..... J [4]

$$E = \frac{1}{2} \frac{Q^2}{C}$$

$$= \frac{1}{2} \cdot \frac{(9.6 \times 10^{-6})^2}{3 \times 10^{-6}}$$

$$\frac{1}{2} QV$$

$$\frac{1}{2} Q \frac{Q}{C} = \frac{1}{2} \frac{Q^2}{C}$$

[Total: 10]

[Turn over

- 6 Two capacitors P and Q, each of capacitance  $C$ , are connected in series with a battery of e.m.f.  $9.0\text{V}$ , as shown in Fig. 6.1.

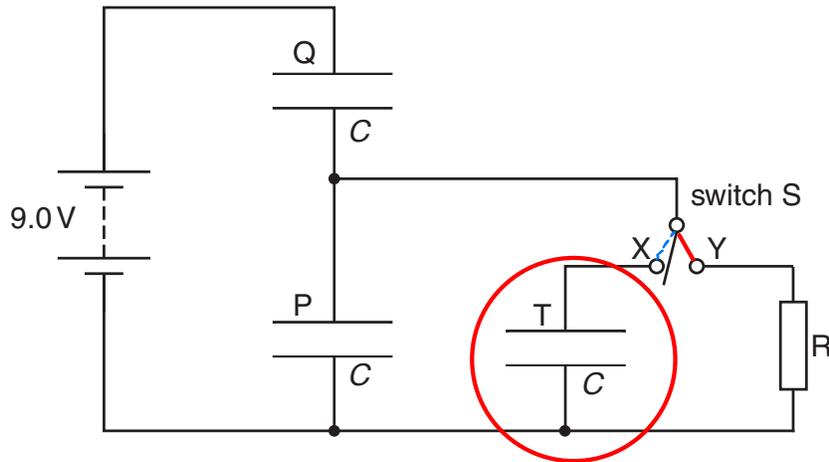


Fig. 6.1

A switch S is used to connect either a third capacitor T, also of capacitance C, or a resistor R, in parallel with capacitor P.

- (a) Switch S is in position X.

Calculate


- (i) the combined capacitance, in terms of C, of the three capacitors,

$$C_T = \left\{ \frac{1}{C+C} + \frac{1}{C} \right\}^{-1} \quad \left( \frac{3}{2C} \right)^{-1}$$

$$\left( \frac{1}{2C} + \frac{1}{C} \right)^{-1}$$

capacitance =  $\frac{2}{3} C$  [2]

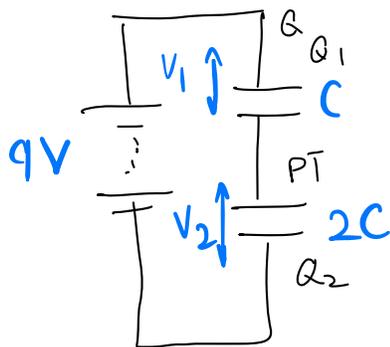- (ii) the potential difference across capacitor Q. Explain your working.



$Q_1 = Q_2$

$C_1 V_1 = C_2 V_2$

$\frac{V_1}{V_2} = \frac{C_2}{C_1} = \frac{2C}{C}$

$V_1 + V_2 = 9V$   
 $2V_2 + V_2 = 9V$   
 $3V_2 = 9V$   
 $V_2 = 3V$

potential difference =  $6.0$  V [2]

6.0

$\frac{V_1}{V_2} = \frac{2}{1} \quad V_1 = 2V_2$

Charge stored in Q is equal to charge stored in combination of P & T.

(b) Switch S is now moved to position Y.


State what happens to the potential difference across capacitor P and across capacitor Q.

capacitor P: p.d decreases from 3.0 V to 0V  
 \* P discharges via R

capacitor Q: p.d increases from 6.0V to 9.0V  
 \* to maintain p.d of 9.0V (power supply) across terminals of battery.

[4]

[Total: 8]

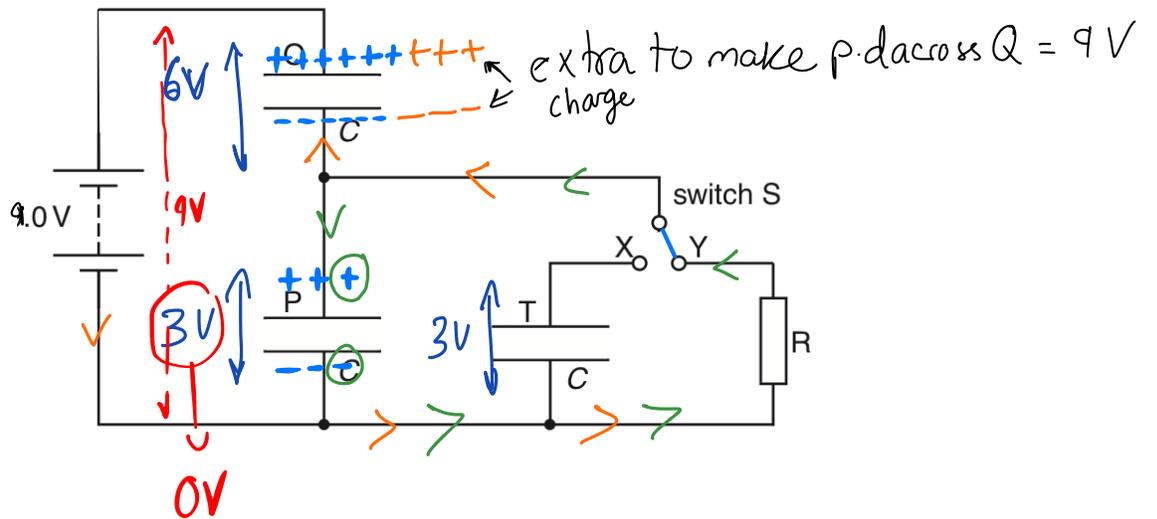

$$C = Q/V$$

7 (a) Define capacitance.

Ratio of charge stored on a single plate of a capacitor to the potential difference across the capacitor. [1]

(b) Three capacitors of capacitances  $C_1$ ,  $C_2$  and  $C_3$  are initially uncharged. They are then connected in series to a battery, as shown in Fig. 7.1.

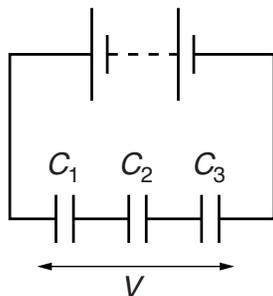


Fig. 7.1

The battery applies a potential difference  $V$  across the three capacitors.

Show that the combined capacitance  $C$  of the capacitors is given by

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$V = V_1 + V_2 + V_3 \quad ; Q = CV \quad ; V = Q/C$$

$$\frac{Q}{C} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3}$$

$$Q = Q_1 = Q_2 = Q_3$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

[2]

(c) A battery of e.m.f. 12V and negligible internal resistance is connected to a network of two capacitors and a resistor, as shown in Fig. 7.2.

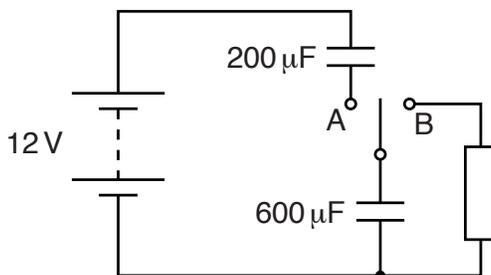



Fig. 7.2

The capacitors have capacitances of  $200\mu\text{F}$  and  $600\mu\text{F}$ . The switch has two positions, A and B.

(i) The switch is moved to position A.

Calculate

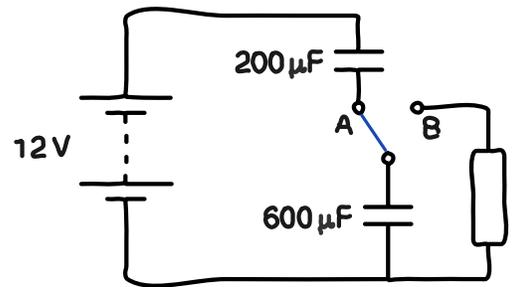1. the combined capacitance of the two capacitors,



$$\left(\frac{1}{C_1} + \frac{1}{C_2}\right)^{-1} = \left(\frac{1}{200} + \frac{1}{600}\right)^{-1}$$


combined capacitance = 150 μF [1]

2. the charge on the 600 μF capacitor,

$$Q = CV$$

$$Q = (150 \times 10^{-6})(12)$$

$$Q = 1.8 \times 10^{-3} \text{ C}$$

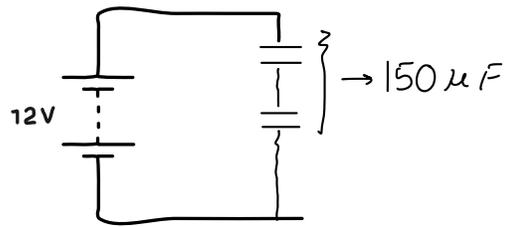

charge = 1.8 × 10<sup>-3</sup> C [1]

*Charge same in Series!*


3. the potential difference across the 600 μF capacitor.

$$V = \frac{Q}{C} = \frac{1.8 \times 10^{-3}}{600 \times 10^{-6}}$$

potential difference = 3.0 V [1]

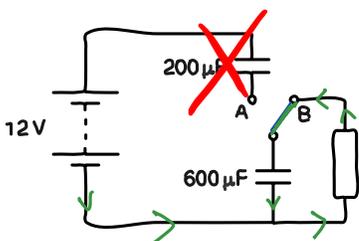(ii) The switch is now moved from position A to position B.

Calculate the potential difference across the 600 μF capacitor when it has discharged 50% of its initial energy.



$$E = \frac{1}{2} CV^2 \quad E \propto V^2$$

$$\frac{E_1}{E_2} = \left(\frac{V_1}{V_2}\right)^2$$

potential difference = 2.0 V [3]

$$\frac{1}{0.5} = \left(\frac{3.0}{V_2}\right)^2 \quad 2 = \frac{9}{V_2^2}$$

[Total: 9]

$$V_2 = \sqrt{\frac{9}{2}}$$

[Turn over

- 6 (a) Define the *capacitance* of a parallel-plate capacitor.


Ratio of charge stored on one plate of the capacitor  
to the potential difference across plates.

[2]

- (b) A student has three capacitors. Two of the capacitors have a capacitance of  $4.0\mu\text{F}$  and one has a capacitance of  $8.0\mu\text{F}$ .

Draw labelled circuit diagrams, one in each case, to show how the three capacitors may be connected to give a total capacitance of:


- (i)  $1.6\mu\text{F}$

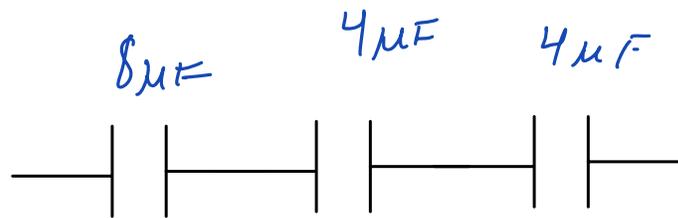

$$\left(\frac{1}{8} + \frac{1}{4} + \frac{1}{4}\right)^{-1} = 1.6\mu\text{F}$$

[1]

- (ii)  $10\mu\text{F}$ .

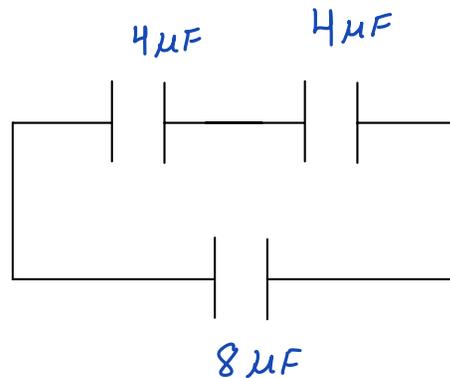

$$\left(\frac{1}{4} + \frac{1}{4}\right)^{-1} + 8 = 10\mu\text{F}$$

[1]

- (c) A capacitor C of capacitance  $47\mu\text{F}$  is connected across the output terminals of a bridge rectifier, as shown in Fig. 6.1.

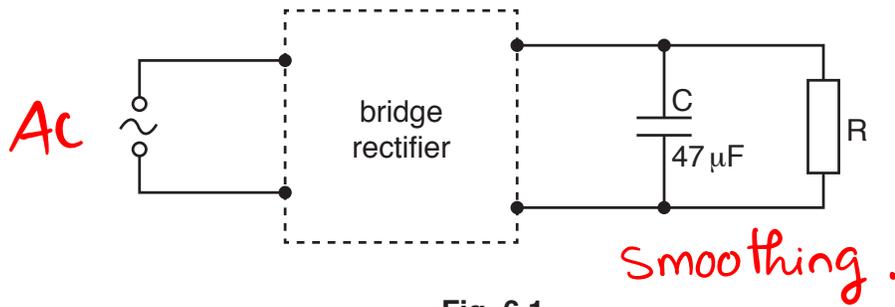


Fig. 6.1

The variation with time  $t$  of the potential difference  $V$  across the resistor R is shown in Fig. 6.2.

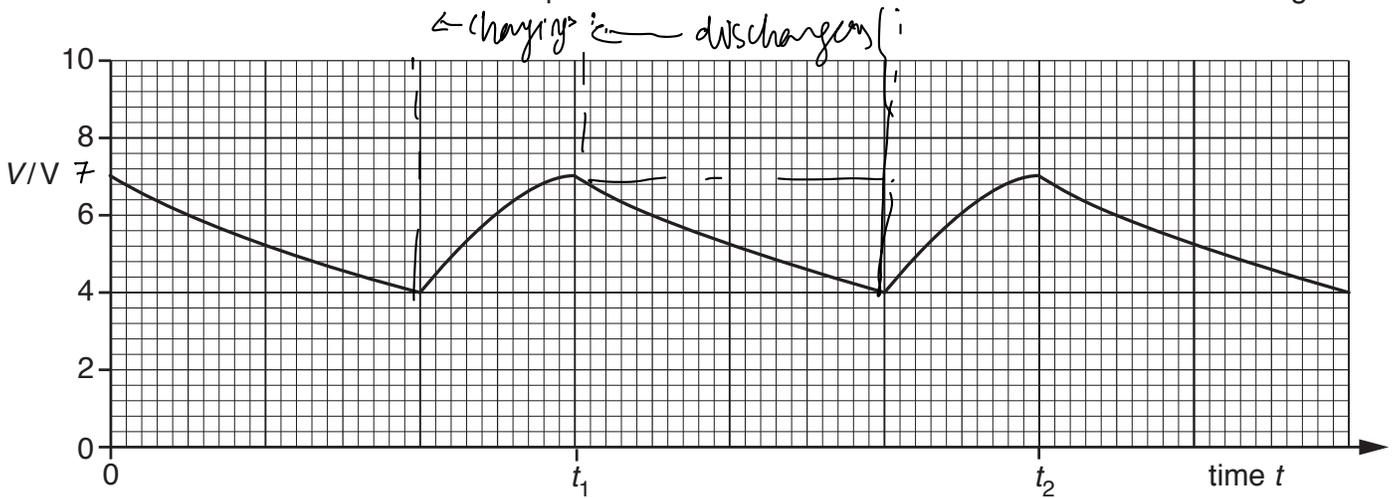


Fig. 6.2

Use data from Fig. 6.2 to determine the energy transfer from the capacitor C to the resistor R between time  $t_1$  and time  $t_2$ .

$$\Delta E = \frac{1}{2} C (V_f^2 - V_i^2)$$

$$\frac{1}{2} (47 \times 10^{-6}) (7^2 - 4^2)$$

energy =  $7.8 \times 10^{-4}$  J [3]

[Total: 7]


4 (a) State two functions of capacitors in electrical circuits.

1. Store energy // smoothing rectified AC

2. Separate charges // preventing sparks.

[2]

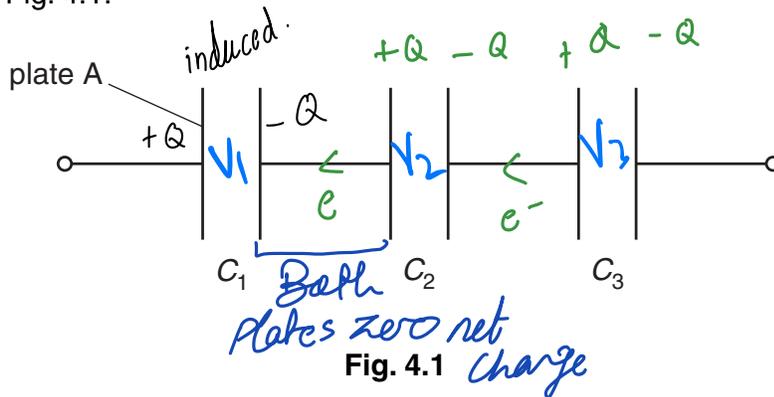(b) Three uncharged capacitors of capacitance  $C_1$ ,  $C_2$  and  $C_3$  are connected in series, as shown in Fig. 4.1.



A charge of  $+Q$  is put on plate A of the capacitor of capacitance  $C_1$ .

(i) State and explain the charges that will be observed on the other plates of the capacitors.

You may draw on Fig. 4.1 if you wish.

-  $Q$  is induced on plate of  $C_1$  opposite to plate A.  
 - by conservation of charge, the charges on each plate, starting from plate A are

$+Q, -Q, +Q, -Q, +Q, -Q$

[2]

(ii) Use your answer in (i) to derive an expression for the combined capacitance of the capacitors.

$C$  in series  $\Rightarrow$

$$Q = CV$$

$$V = \frac{Q}{C}$$

$$V_T = V_1 + V_2 + V_3$$

$$\frac{Q}{C_T} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3} \quad ; \text{ since } Q_1 = Q_2 = Q_3 = Q$$

[2]

$$\frac{1}{C_{Total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

(c) A capacitor of capacitance  $12\mu\text{F}$  is charged using a battery of e.m.f.  $9.0\text{V}$ , as shown in Fig. 4.2.

For  
Examiner's  
Use


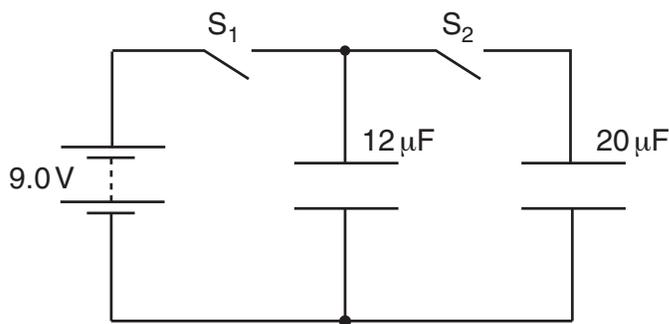


Fig. 4.2

Switch  $S_1$  is closed and switch  $S_2$  is open.

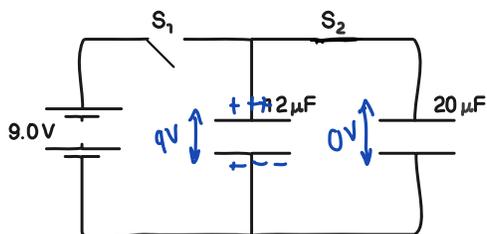- (i) The capacitor is now disconnected from the battery by opening  $S_1$ . Calculate the energy stored in the capacitor.



$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} (12 \times 10^{-6}) (9)^2$$

$q$  flow to  $20\mu\text{F}$   $Q = CV$   
 $= 12 \times 9$   
 $V_{12\mu\text{F}} = V_{20\mu\text{F}} = 108\mu\text{C}$

energy =  $4.86 \times 10^{-4}$  J [2]

- (ii) The  $12\mu\text{F}$  capacitor is now connected to an uncharged capacitor of capacitance  $20\mu\text{F}$  by closing  $S_2$ . Switch  $S_1$  remains open. The total energy now stored in the two capacitors is  $1.82 \times 10^{-4}\text{J}$ .

Suggest why this value is different from your answer in (i).

There is energy dissipated due to resistance of wires / as sparks. [1]

- 5 The variation with potential difference  $V$  of the charge  $Q$  on one of the plates of a capacitor is shown in Fig. 5.1.

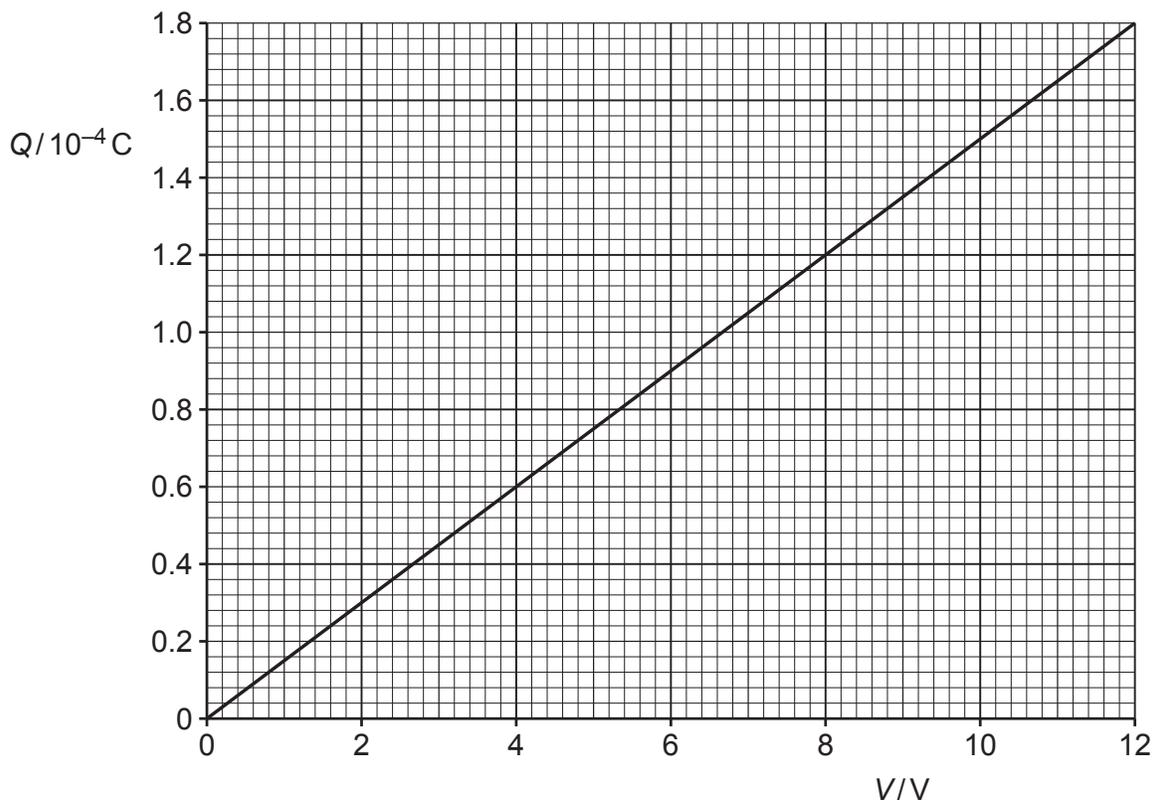


Fig. 5.1

The capacitor is connected to an 8.0V power supply and two resistors R and S as shown in Fig. 5.2.

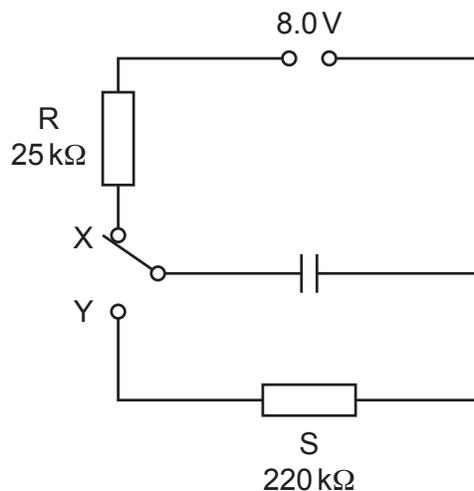


Fig. 5.2

The resistance of R is 25 kΩ and the resistance of S is 220 kΩ.

The switch can be in either position X or position Y.

- (a) The switch is in position X so that the capacitor is fully charged.

Calculate the energy  $E$  stored in the capacitor.

$$E = \frac{1}{2} QV$$

$$= \frac{1}{2} (1.2 \times 10^{-4}) (8)$$

$$E = 4.08 \times 10^{-4} \text{ J [2]}$$


- (b) The switch is now moved to position Y.

- (i) Show that the time constant of the discharge circuit is 3.3 s.

$$\tau = RC$$

$$= (220 \times 10^3) (1.5 \times 10^{-5})$$

$$= 3.3 \text{ s}$$

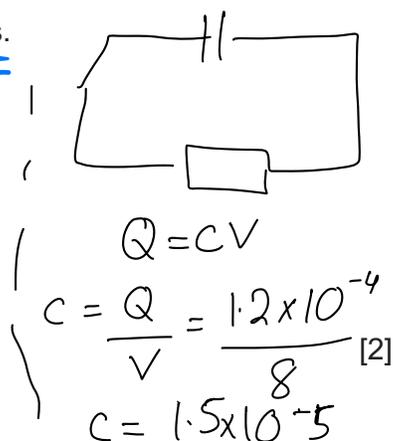

- (ii) The fully charged capacitor in (a) stores energy  $E$ .

Determine the time  $t$  taken for the stored energy to decrease from  $E$  to  $E/9$ .

discharge equation.

from  $E = \frac{1}{2} CV^2$

$$E \propto V^2$$

$$\frac{E_1}{E_2} = \left( \frac{V_1}{V_2} \right)^2$$

$$\frac{E}{E/9} = \left( \frac{8.0}{V} \right)^2$$

$$9 = \left( \frac{8}{V} \right)^2$$

$$V = \frac{8}{3}; \frac{V_0}{3}$$

$$V = V_0 e^{-t/RC}$$

$$\frac{8}{3} = e^{-t/RC} \text{ or } \frac{V_0}{3} = V_0$$

$$\frac{1}{3} = e^{-t/RC}$$

$$\ln\left(\frac{1}{3}\right) = -\frac{t}{3.3}$$

$$t = 3.63 \text{ s}$$

$$E = \frac{1}{2} CV^2 = C \cdot \text{constant}$$

$$E \propto V^2$$

$$3.6$$

$$t = 3.6 \text{ s [4]}$$

$$Q = CV$$

$$Q \propto V$$

$$V = IR$$

$$V \propto I$$

$$Q = Q_0 e^{-t/RC}$$

$$V = V_0 e^{-t/RC}$$

$$I = I_0 e^{-t/RC}$$

- (c) A second identical capacitor is connected in parallel with the first capacitor.

State and explain the change, if any, to the time constant of the discharge circuit.

Total capacitance is doubled, hence time constant is also doubled.

[2]

[Total: 10]

$$\begin{array}{c} \uparrow \tau = RC \uparrow \\ \times 2 \qquad \qquad \times 2 \end{array}$$