

PROSPERITY ACADEMY

A2 PHYSICS 9702

Crash Course

RUHAB IQBAL

ALTERNATING CURRENTS

COMPLETE NOTES









0331 - 2863334



**ruhab.prosperityacademics
@gmail.com**


Direct Current:- The current is always in one direction

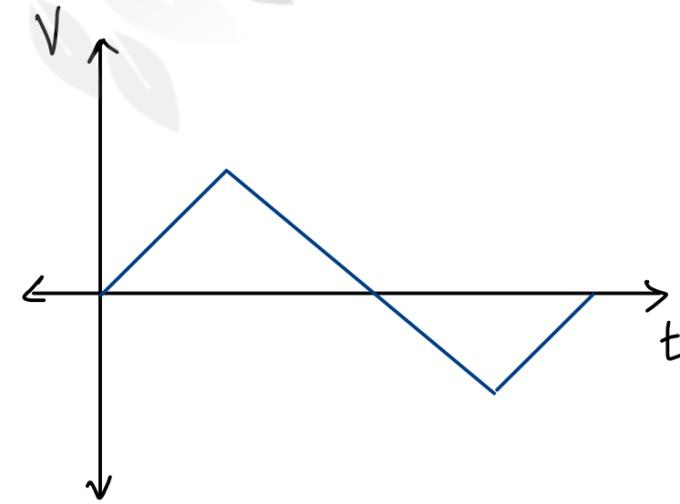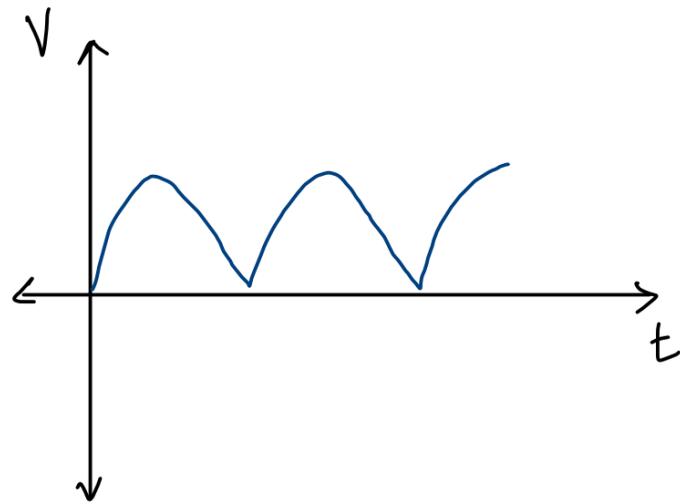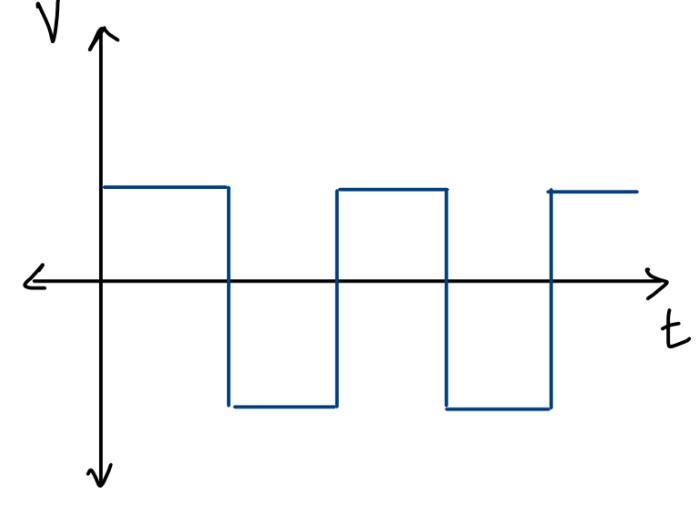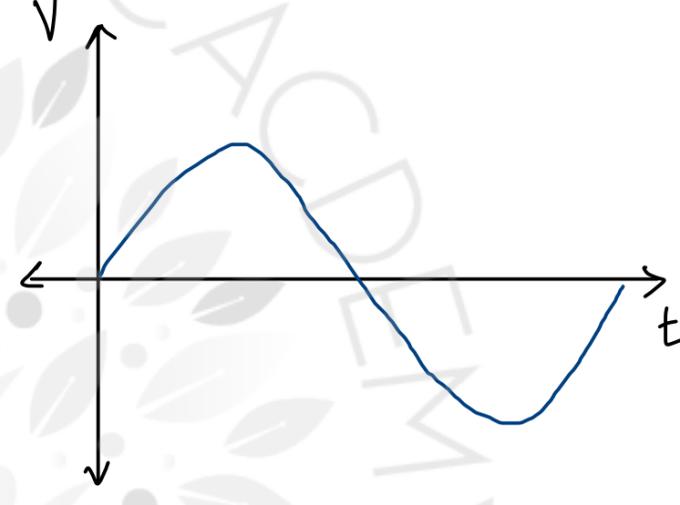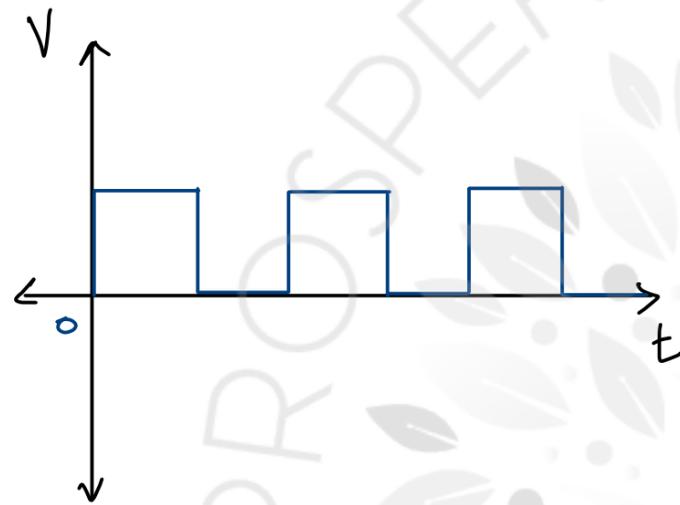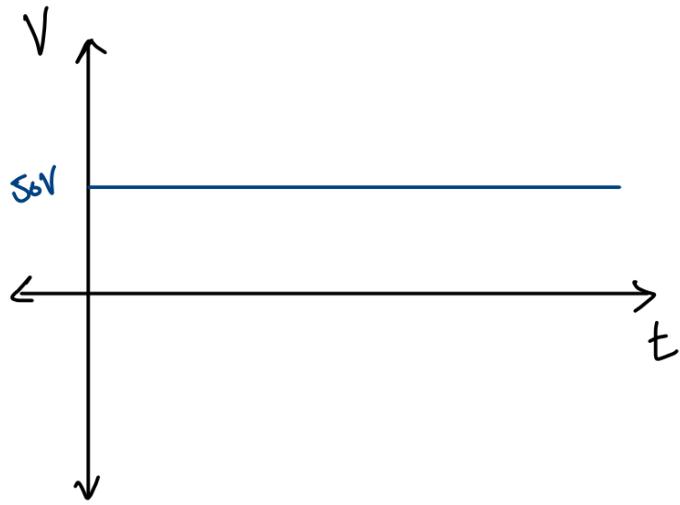Alternating Currents:- The current is switching its direction of flow.



Sinusoidal Alternating Currents:-

$$V = V_0 \sin(\omega t)$$

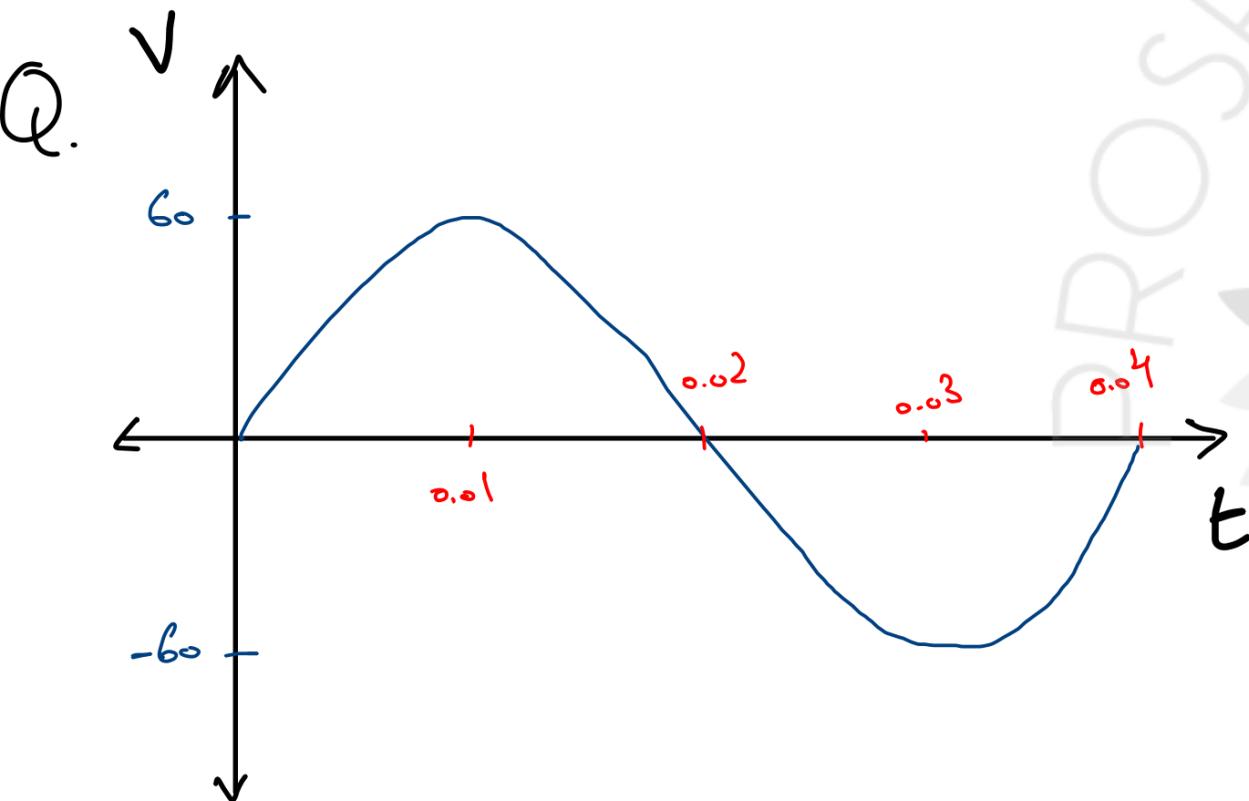

$$V = 60 \sin(\omega t)$$

$$\omega = \frac{2\pi}{T} \Rightarrow \omega = \frac{2\pi}{0.04} = 50\pi$$

$$V = 60 \sin(50\pi t) \quad \text{or} \quad V = 60 \sin(157t)$$


Q. $I = 5 \sin(1000t)$

$$I_0 = 5$$


$$\omega = 1000$$

$$\frac{2\pi}{T} = 1000$$
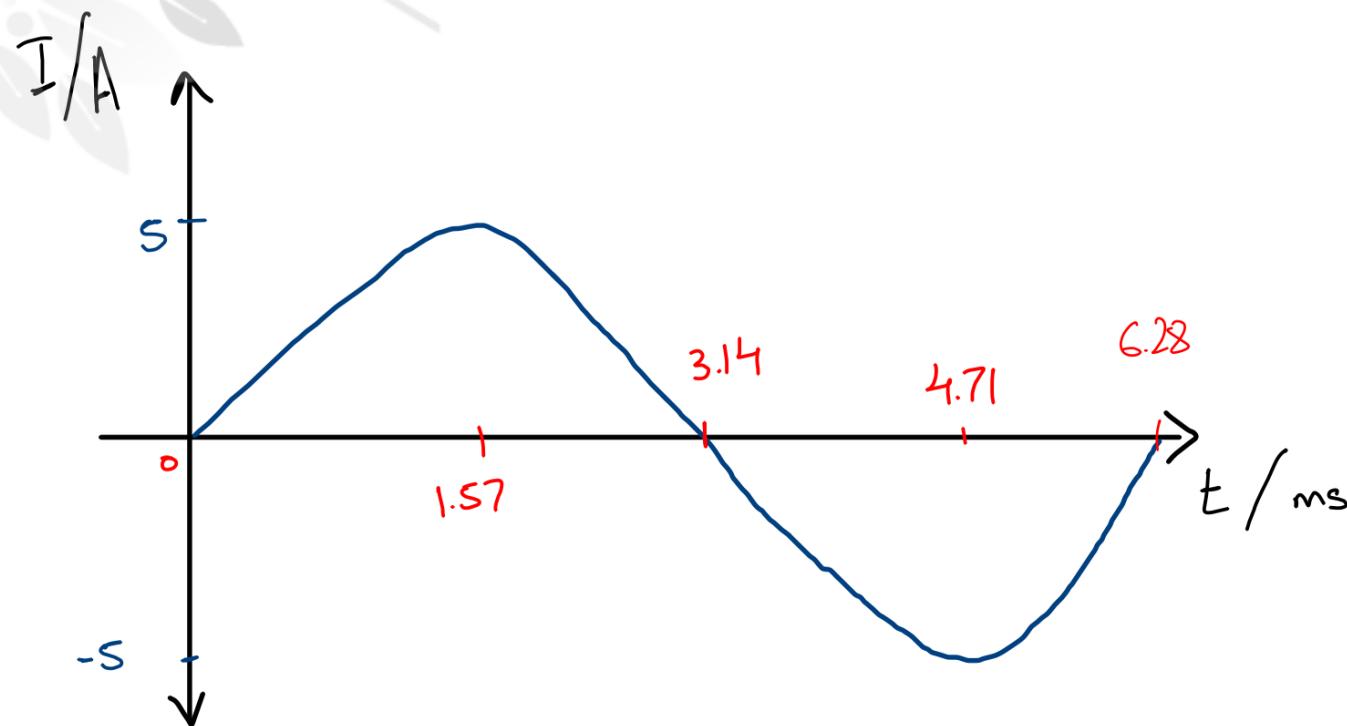
$$T = \frac{2\pi}{1000} = 6.28 \times 10^{-3}$$



Root mean square :-

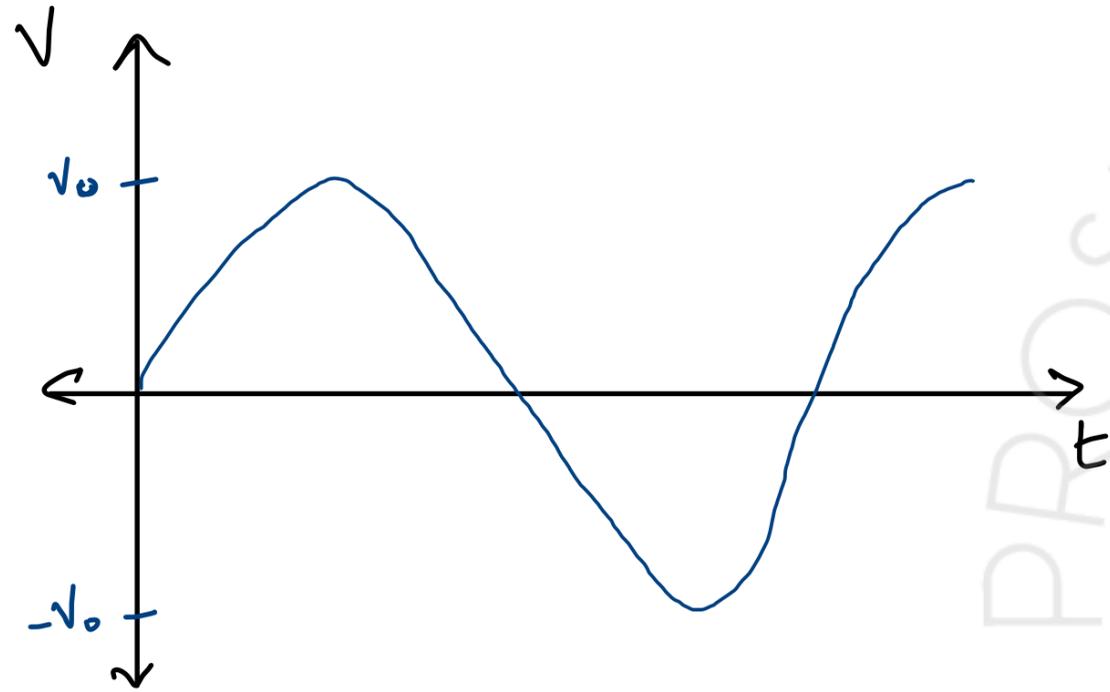

Mean Voltage = 0
Mean Current = 0

$$V_{r.m.s} = \frac{V_0}{\sqrt{2}}$$

$$I_{r.m.s} = \frac{I_0}{\sqrt{2}}$$

Charge :-

$$Q = I_{r.m.s} \times t$$


Ohm's law :-

$$V_{r.m.s} = R \times I_{r.m.s}$$

Power :-

$$P = I_{r.m.s} \times V_{r.m.s}$$

Square wave R.M.S. Voltage:-

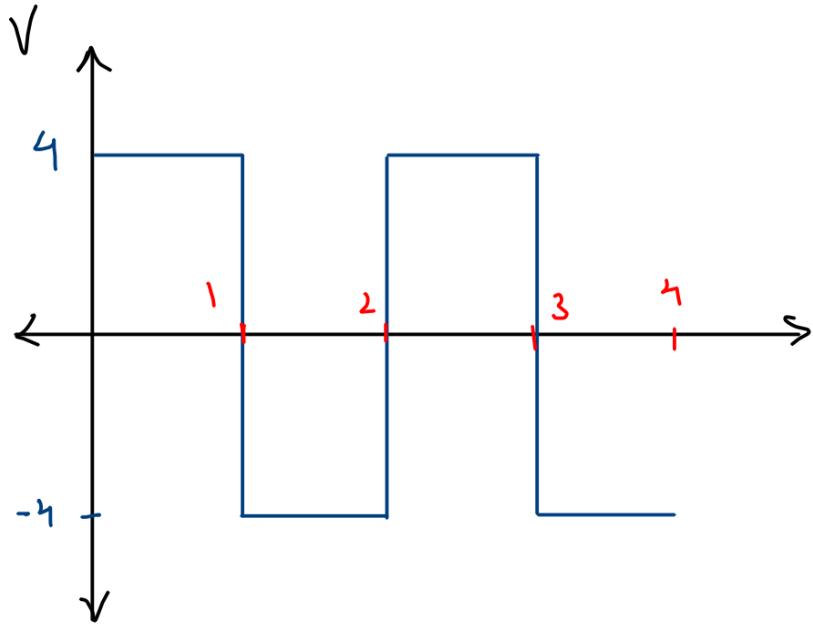

$$T = 2s$$

$$+4 \text{ for } \frac{1}{2}T$$

$$-4 \text{ for } \frac{1}{2}T$$

$$= \left(\text{Positive}^2 \text{ voltage} \times \text{fraction of time} \right) + \left(\text{negative}^2 \text{ voltage} \times \text{fraction of time} \right)$$




$$V_{r.m.s} = \sqrt{\left[4^2 \times \frac{1}{2} \right] + \left[-4^2 \times \frac{1}{2} \right]}$$

$$= \sqrt{8 + 8}$$



$$V_{r.m.s} \text{ of square wave} = 4$$

Conversion of AC to DC:- (Rectification)

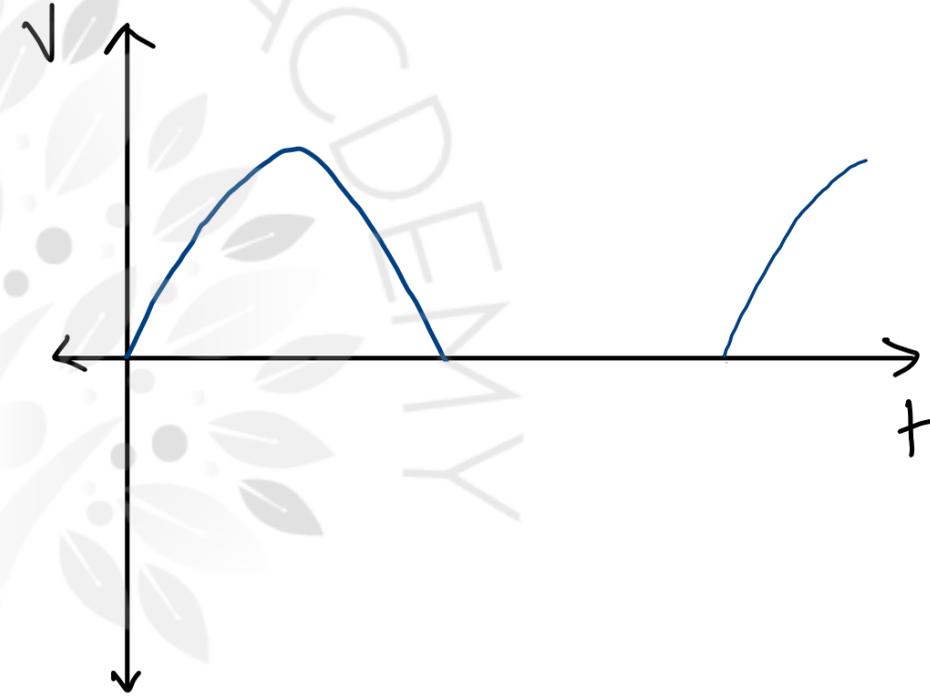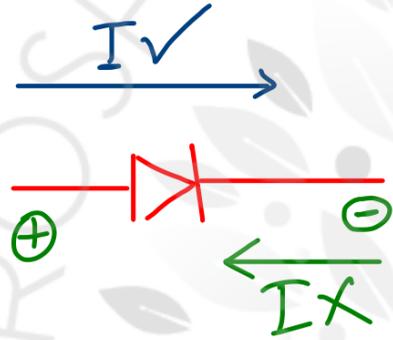
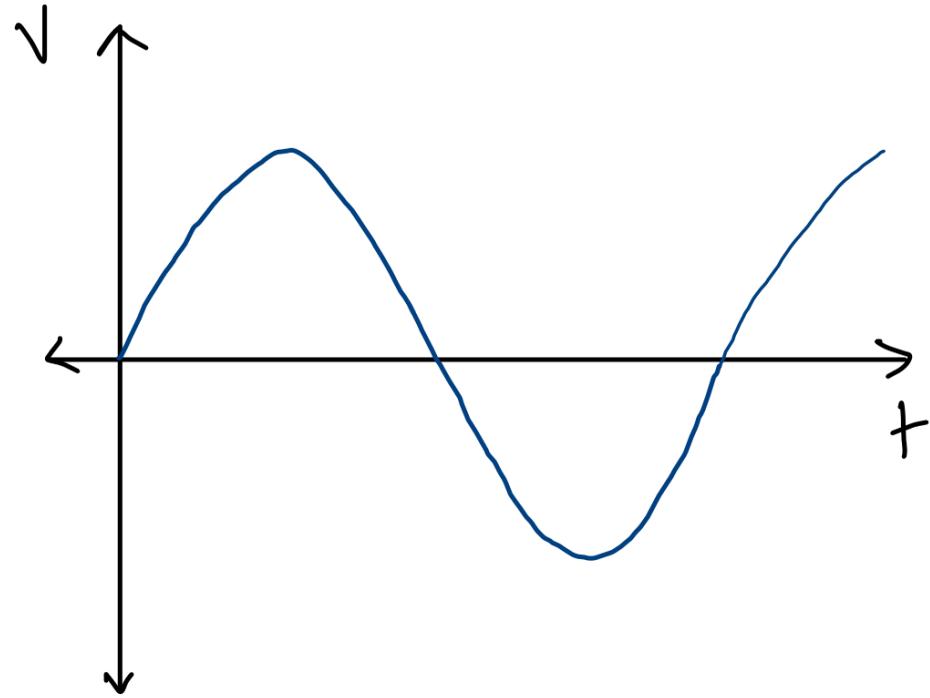
Half wave rectification:- (Gives half amount of power)



Full bridge Rectifier:-

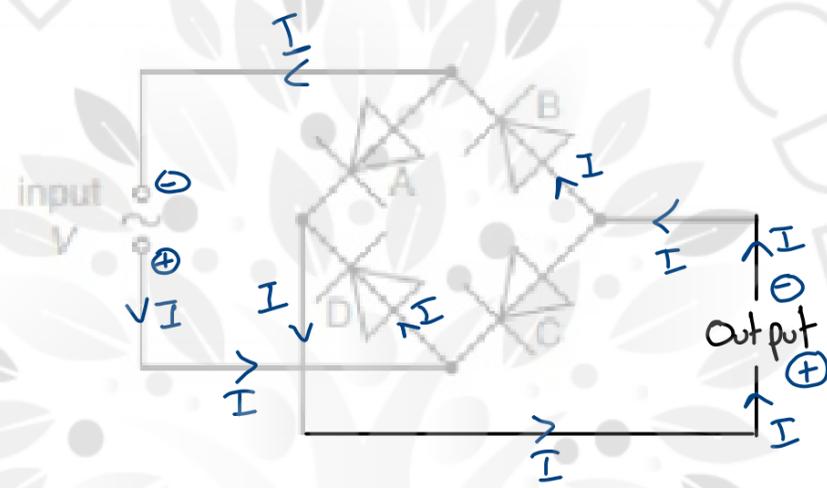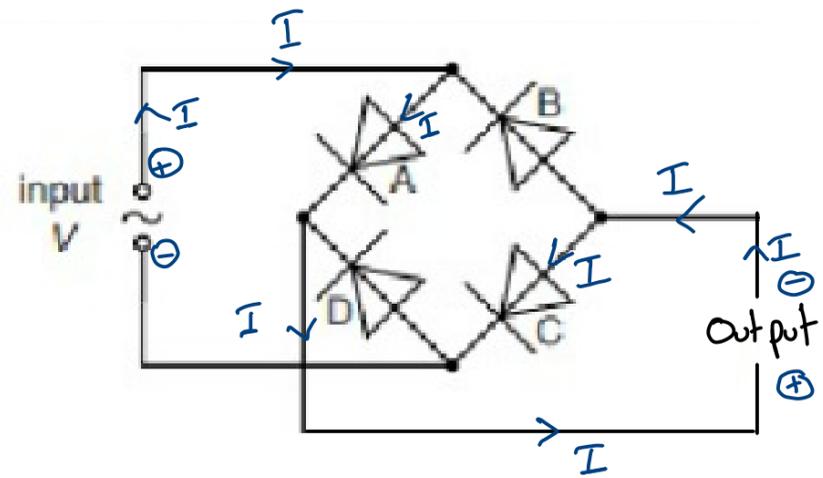

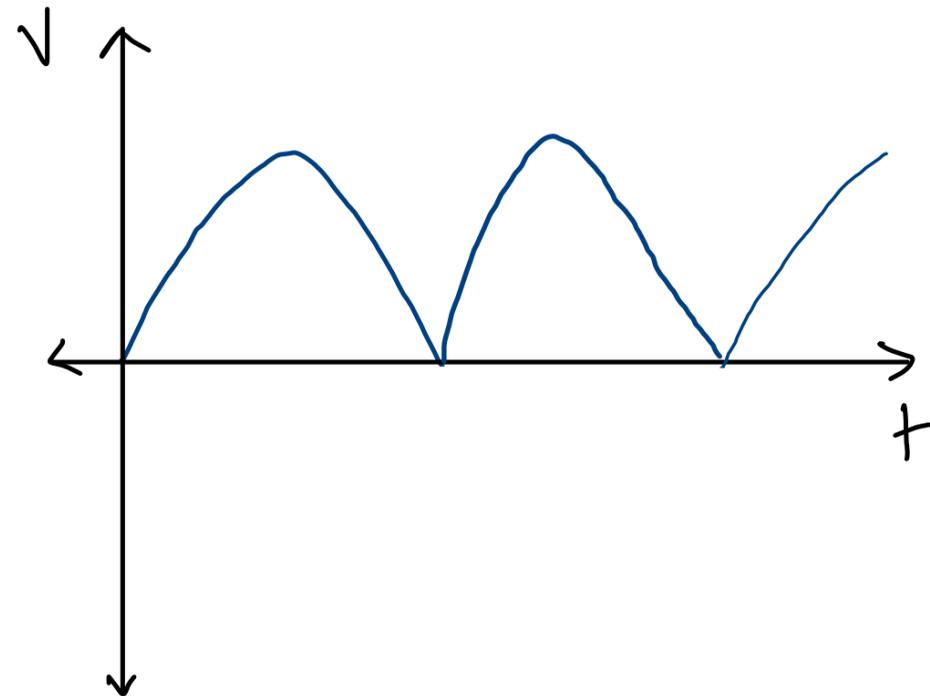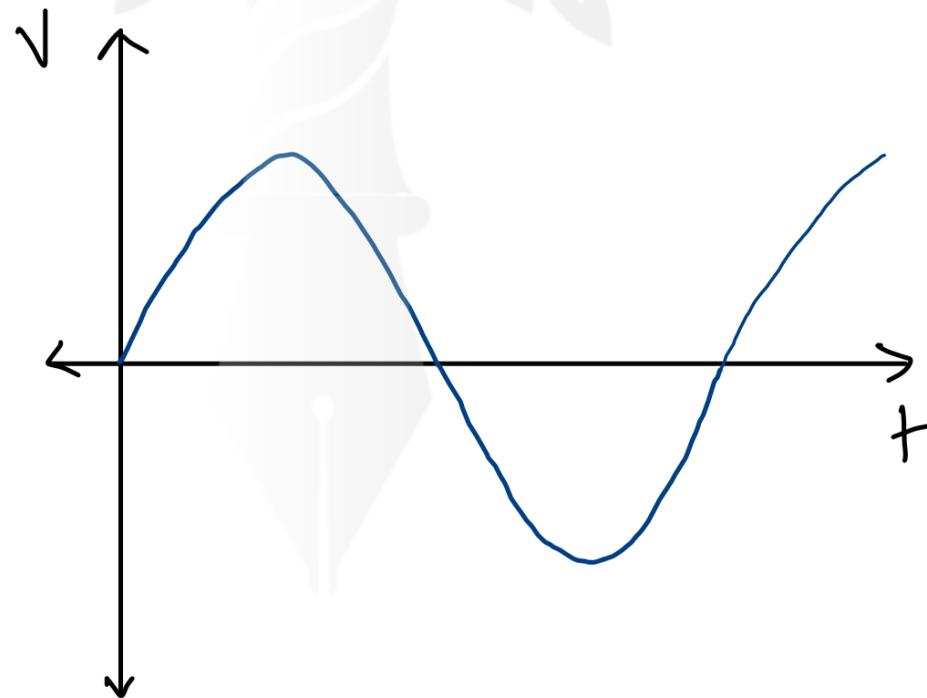- 1) Remember the diagram
- 2) Be able to mark +ve & -ve on load.
- 3) Make path of current



- 11 The variation with time t of the sinusoidal current I in a resistor of resistance 450Ω is shown in Fig. 11.1.

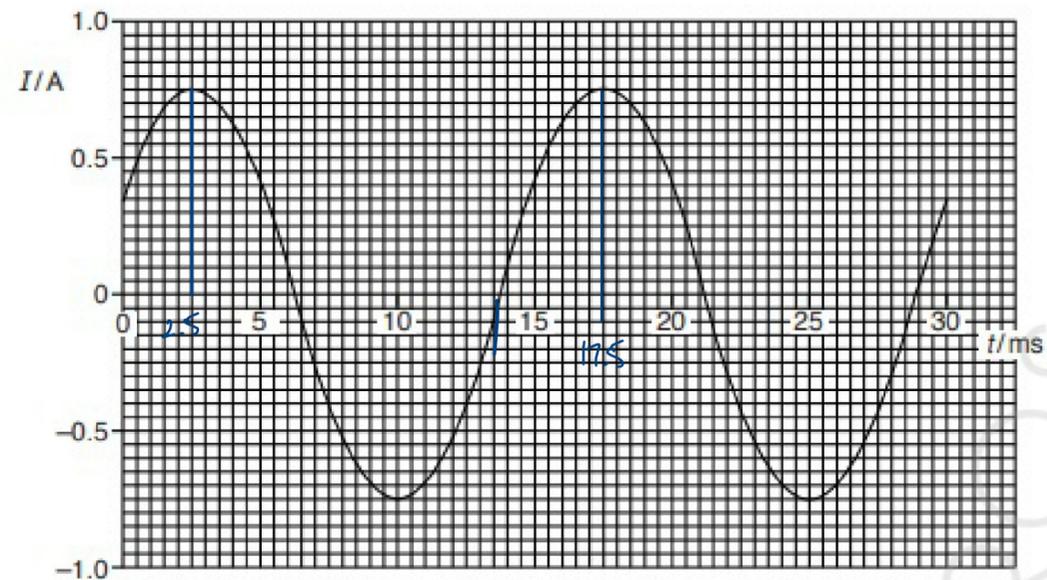


Fig. 11.1

Use data from Fig. 11.1 to determine, for the time $t = 0$ to $t = 30$ ms,

- (a) the frequency of the current,

$$T = 17.5 - 2.5 = 15 \text{ ms} \quad f = \frac{1}{15 \times 10^{-3}}$$

frequency = 67 Hz [2]

- (b) the mean current,

mean current = 0 A [1]

- (c) the root-mean-square (r.m.s.) current,

$$I_{\text{r.m.s.}} = \frac{I_0}{\sqrt{2}} = \frac{0.75}{\sqrt{2}} = 0.53$$

r.m.s. current = 0.53 A [2]

- (d) the energy dissipated by the resistor.

$$\begin{aligned} E &= I_{\text{r.m.s.}}^2 \times R \times t \\ &= (0.53)^2 \times 450 \times (30 \times 10^{-3}) \\ &= 3.8 \end{aligned}$$

energy = 3.8 J [2]

[Total: 7]

11 A bridge rectifier contains four ideal diodes A, B, C and D, as shown in Fig. 11.1.


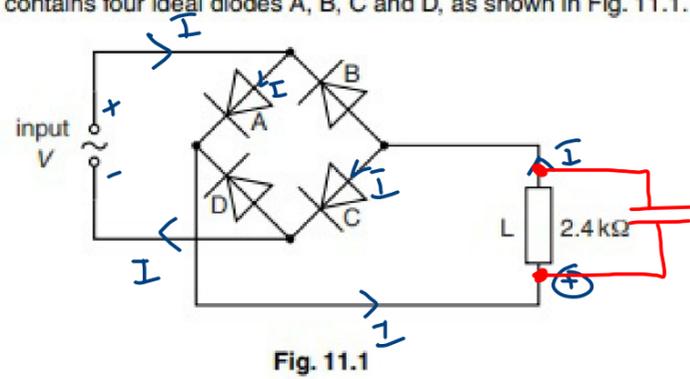


Fig. 11.1

The output of the rectifier is connected to a load L of resistance 2.4 kΩ.

(a) On Fig. 11.1, mark with the letter P the positive terminal of the load. [1]

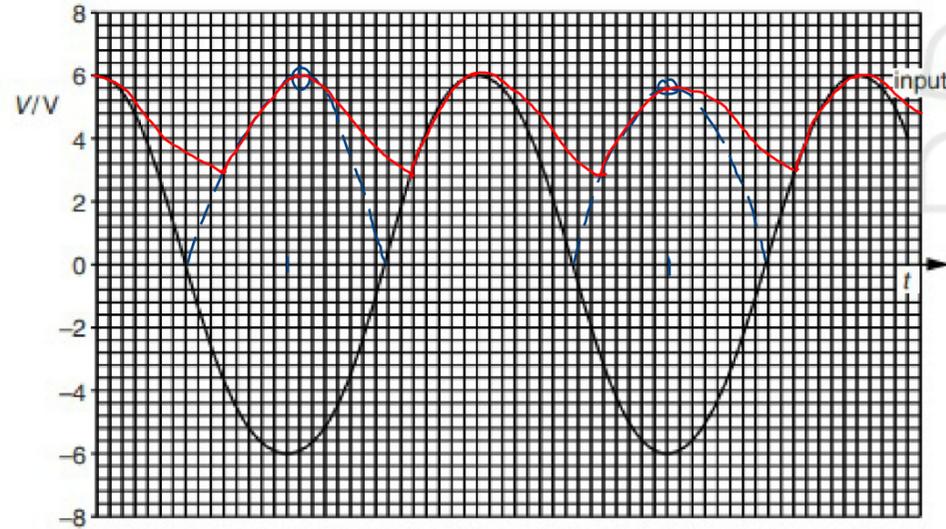(b) The variation with time t of the potential difference V across the input to the rectifier is shown in Fig. 11.2.



Calculate the root-mean-square (r.m.s.) current in the load L.

$$V_{r.m.s} = I_{r.m.s} \times R$$

$$\frac{6}{\sqrt{2}} = I_{r.m.s} \times (2.4 \times 10^3)$$

$$I_{r.m.s} = 1.77$$

r.m.s. current = 1.8 A [2]

(c) The potential difference across the load L is to be smoothed using a capacitor.

(i) On Fig. 11.1, draw the symbol for a capacitor, connected to produce smoothing. [1]

(ii) The minimum potential difference across the load L with the smoothing capacitor connected is 3.0 V.

On Fig. 11.2, sketch the variation with time t of the potential difference across the load L. [3]

[Total: 7]

Handwritten note: A capacitor symbol is drawn in parallel with the load resistor. The text says "parallel with load".

- 7 (a) Alternating current (a.c.) is converted into direct current (d.c.) using a full-wave rectification circuit. Part of the diagram of this circuit is shown in Fig. 7.1.

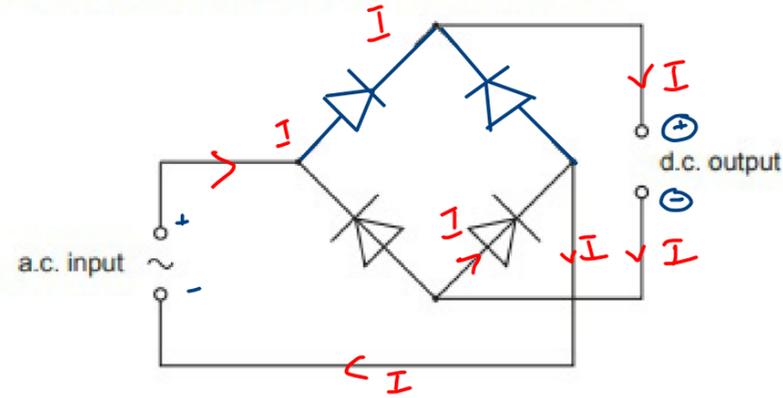


Fig. 7.1

- (ii) The supply is connected to a $12\ \Omega$ resistor. Calculate the mean power dissipated in the resistor.

$$P = \frac{V_{r.m.s}^2}{R} = \frac{\left(\frac{3.75}{\sqrt{2}}\right)^2}{12}$$

mean power = 0.59 W [2]

[Total: 6]

- (i) Complete the circuit in Fig. 7.1 by adding the necessary components in the gaps. [1] ✓
 (ii) On Fig. 7.1 mark with a + the positive output terminal of the rectifier. [1] ✓

- (b) The output voltage V of an a.c. power supply varies sinusoidally with time t as shown in Fig. 7.2.

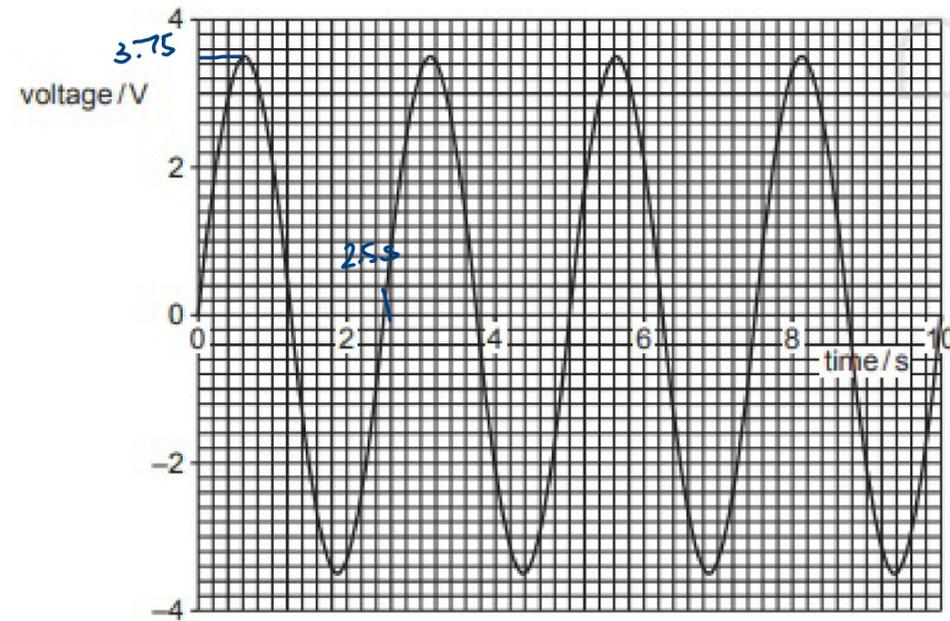


Fig. 7.2

- (i) Determine the equation for V in terms of t , where V is in volts and t is in seconds.

$$V = V_0 \sin(\omega t) \Rightarrow V = 3.75 \sin\left(\frac{2\pi}{2.5} t\right)$$

$V = 3.75 \sin(0.8t)$ [2]