

# DC Circuits

## Electromotive Force

- It is the energy transformed from chemical to electrical energy per unit charge
- It is measured in Volts
- It is also the potential difference across a battery when no current is flowing

## Internal Resistance

- All power supplies have resistance between their terminals, known as internal resistance
- It causes some electrical energy to dissipate from the power supply
- It causes a loss of voltage
- Terminal potential difference ( $V_R$ ) is the voltage across the components of a circuit
- $V_R = IR$
- When current passes through the cell, voltage produces across the internal resistance
- The voltage is not available to the rest of the circuit and is known as lost volts ( $V_r$ )
- $V_r = Ir$
- $V_r = E - V_R$
- $E = IR + Ir$

## Kirchhoff's First Law

- The sum of currents entering a junction is equal to the sum of currents leaving the junction
- This is due to the conservation of charge

## Kirchhoff's Second Law

- The sum of e.m.f.s in a closed circuit is equal to the sum of potential differences across individual components
- This is due to the conservation of energy
- In series circuit, voltage splits across components depending on the resistance
- The total e.m.f. is equal to the sum of voltages
- In a parallel circuit, the voltage across each loop is same
- The sum of voltages in each closed loop is equal to the total e.m.f.

## Resistors in Series

- In series circuit, the total resistance is the sum of all individual resistances
- The equation is derived through Kirchhoff's laws

$$V = V_1 + V_2$$

$$IR = IR_1 + IR_2$$

$$R = R_1 + R_2 \dots$$

### Resistors in Parallel

→ In parallel circuits, the reciprocal of the total resistance is equal to the sum of the reciprocal of the individual resistances

→ The equation is derived through Kirchhoff's laws

$$I = I_1 + I_2$$

$$V/R = V/R_1 + V/R_2$$

$$1/R = 1/R_1 + 1/R_2 \dots$$

For two resistors:  $R = R_1 R_2 / (R_1 + R_2)$

### Potential Dividers

→ Potential difference is divided across two resistors connected in series

→ Potential dividers produce an output voltage as a fraction of the input voltage

$$\rightarrow V_{\text{out}} = \frac{R_2}{R_1 + R_2} V_{\text{in}}$$

→ The  $V_{\text{out}}$  is measured across  $R_2$

→ The resistor with the larger resistance will have greater potential difference

→ If a resistor's resistance is increased, it will get more potential difference and the other will get lesser

→ Variable resistors such as LDRs and thermistors can be used to vary the output voltage

### Potentiometer

→ It is a variable resistor

→ It is used in potential dividers to give variable output voltages

→ The symbol has an arrow with the resistor

→ It consists of a coil of wire with a sliding contact

→ Moving the slider changes the length of the coil the current passes through and thus, the resistance

### Galvanometer

→ It is a sensitive instrument to detect electric current

→ It is used in a potentiometer to measure the e.m.f. between two points

→ It has an arrow/needle which deflects in the direction of the current

→ If the arrow is facing upwards, there is no current, or null deflection

→ According to Ohm's law, there will be no current when there is no voltage

→ The potential difference across the galvanometer will be zero when the potential on both sides of it is equal

→ This occurs when the position of the sliding contact produces a voltage equal to the e.m.f.

→ The potential of the cell should oppose the e.m.f. in the circuit

→ Positive terminals should be connected together

→ The sliding contact is adjusted till the galvanometer gives null reading

→ There is no current due to the opposing equal voltage and e.m.f.

$$\rightarrow V_1/L_1 = V_2/L_2$$